

Unit - 2.

Op-Amp as a voltage comparator:-


→ It is a circuit used to compare the input voltages of an op-amp.

→ It is an open loop op-amp.

→ Comparator is also called as square wave generator.

Inverting comparator:-

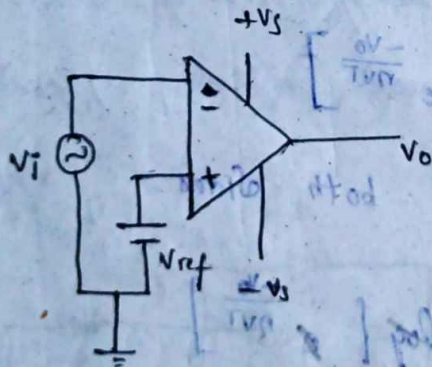→ If input voltage is given to the inverting terminal and reference voltage is given non-inverting terminal then it is called inverting comparator.



→ Compare the input voltages V_{in} & V_{ref} then it produces output either +ve or -ve saturation voltage.

Case - 1:-

$$V_{in} > V_{ref}$$

$$V_{id} = V_{ref} - V_{in}$$

$$V_{id} = 0.8 - 1$$

$$= -0.2$$

$$V_{id} = -V_e$$

$$V_o = -V_e$$

$$V_o = -V_{sat}$$

Case - 2'

$$V_{in} < V_{ref}$$

$$V_{id} = V_{ref} - V_{in}$$


$$V_{id} = 0.3 - 0.2$$

$$V_{id} = 0.1$$

$$V_{id} = +V_e$$

$$V_o = +V_e$$

$$V_o = +V_{sat}$$

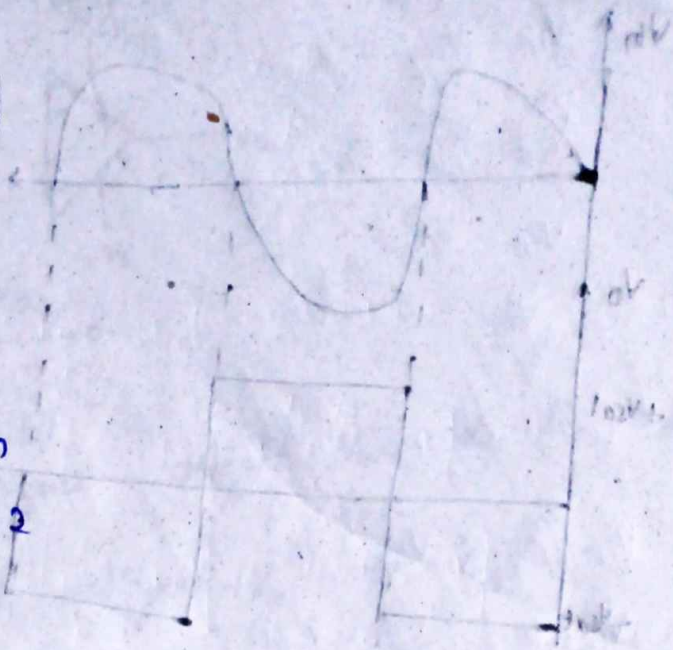


Case - 3'

$$V_{in} = V_{ref}$$

$$V_{id} = V_{ref} - V_{in}$$

$$V_{id} = 0$$

$$V_o = 0$$

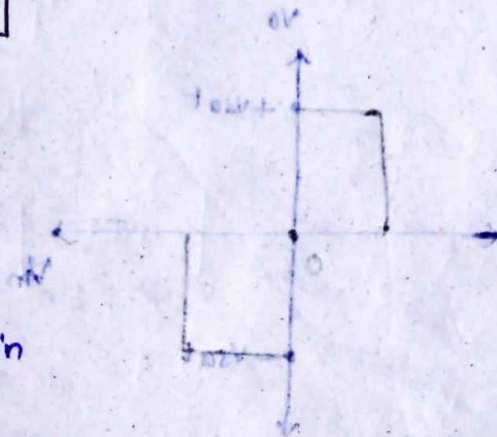


Let us assume $V_{ref} = 0$

$$1) V_{in} > 0 ; V_o = -V_{sat}$$

$$2) V_{in} < 0 ; V_o = +V_{sat}$$

$$3) V_{in} = 0 ; V_o = 0$$

wave form:-

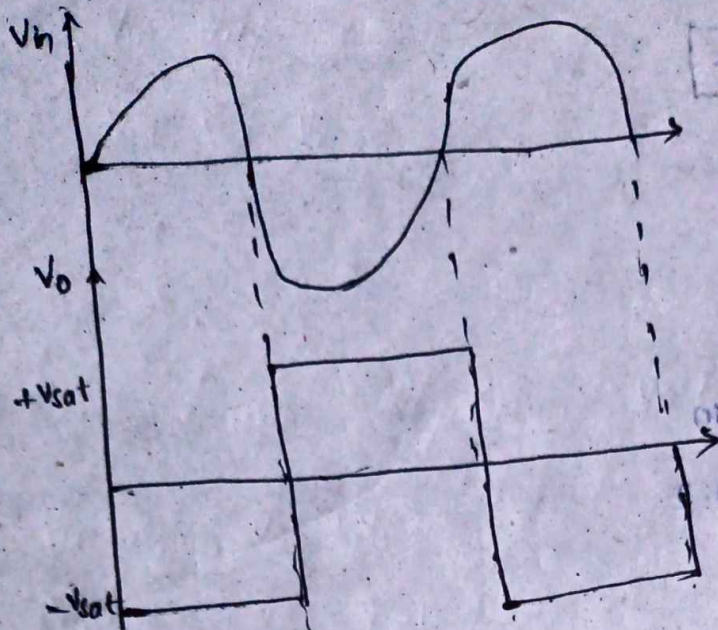

$$1.0V - 0V = 0V$$

$$0V - 0V = 0V$$

$$0V - 0V = 0V$$

$$0V - 1.0V = -1.0V$$

$$0 - 1.0 = -1.0$$

$$1.0 = 1.0$$

$$0V - 0V = 0V$$

$$0V - 0V = 0V$$

$$1.0V + 0V = 1.0V$$

$$1.0 - 0 = 1.0$$


$$0V - 0V = 0V$$

$$0V - 1.0V = -1.0V$$

$$0 = 0$$

$$0 = 0V$$

Transfer Curve:-

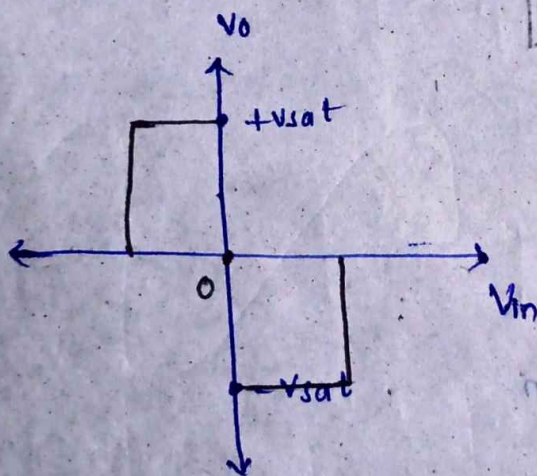

$$0V - 0V = 0V$$


$$0V - 1.0V = -1.0V$$

$$0 = 0$$

$$0 = 0V$$

Non-Inverting comparator:-

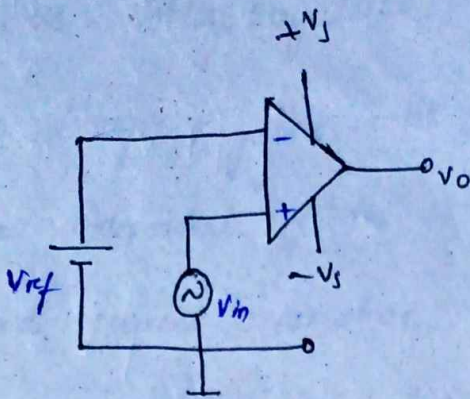→ If Input voltage is given to the non-inverting terminal and reference voltage is given to the inverting terminal then it is called as non-inverting comparator.



$V_{in} = 5V$
 $V_{ref} = 0.3V$
 $V_{id} = V_{in} - V_{ref}$
 $V_{id} = 5V - 0.3V = 4.7V$
 $V_{id} > 0$
 $V_o = +V_{sat}$

→ Compare the input voltages V_{in} and V_{ref} then it produces output voltages $+V_{sat}$ and $-V_{sat}$.

Case - 1 :- $V_{in} > V_{ref}$

$$V_{in} = 5V$$

$$V_{ref} = 0.3V$$


$$V_{id} = V_{in} - V_{ref}$$

$$= 5 - 0.3 = 4.7V$$

$$V_{id} = +ve$$

$$V_o = +ve$$

$$V_o = +V_{sat}$$

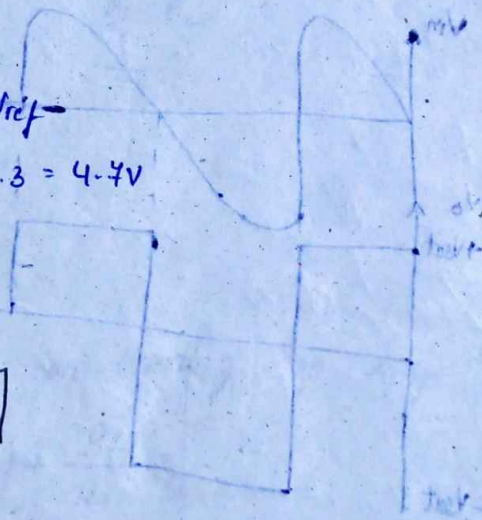

Case - 2 :- $V_{in} < V_{ref}$

$$V_{ref} = 0.3$$

$$V_{in} = 0.1$$


$$V_{id} = V_{in} - V_{ref}$$

$$= 0.1 - 0.3 = -0.2$$

$$V_{id} = -ve$$

$$V_o = -ve$$

$$V_o = -V_{sat}$$

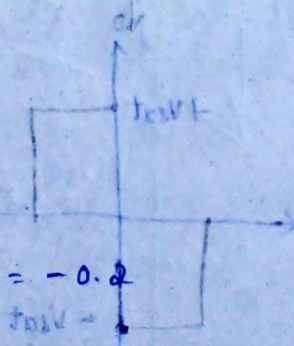


Case (iii): -

$$V_{in} = V_{ref}$$

$$V_{id} = V_{in} - V_{ref}$$

$$V_{id} = 0$$

$$V_o = 0$$

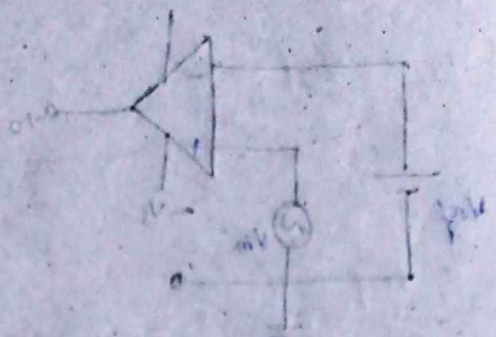


Let us assume reference voltage = 0

1) $V_{in} > 0 ; V_o = +V_{sat}$


2) $V_{in} < 0 ; V_o = -V_{sat}$

3) $V_{in} = 0 ; V_o = 0$

Wave form:-

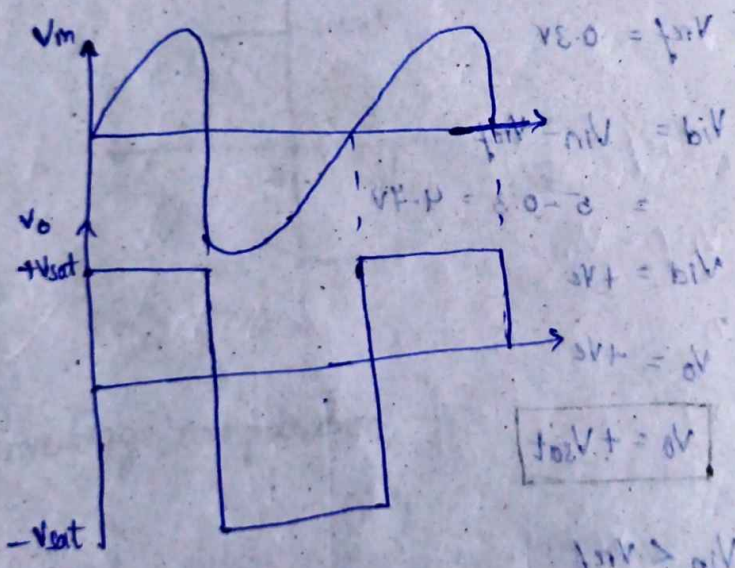


Transfer curve:-

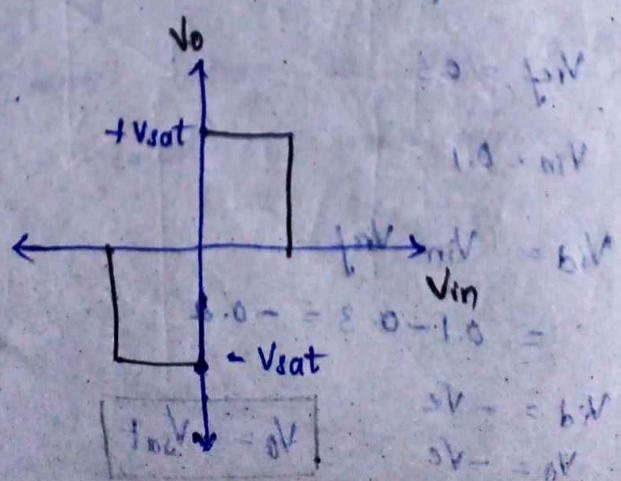

Op-Amp as Voltage regulator:-

In voltage regulator the output voltage V_o should be independent of the input voltage variation and load current variation.

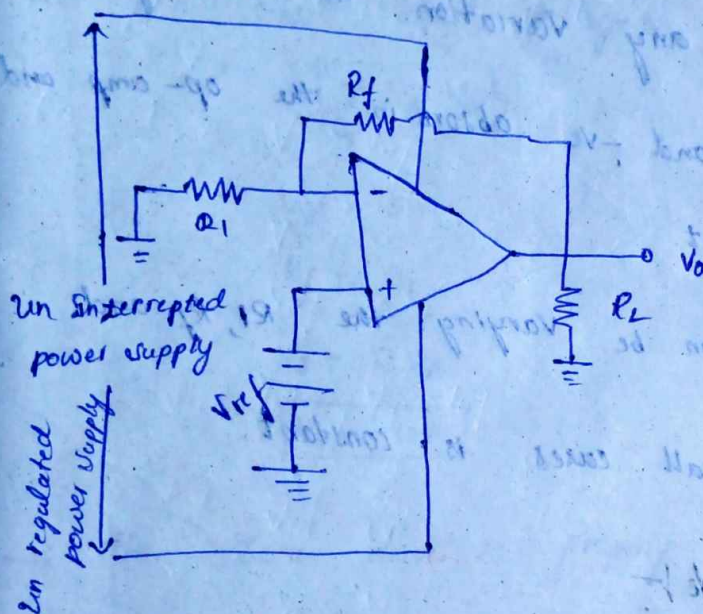→ If reference voltage is fixed then output voltage show in the below circuit.




The gain of the non-inverting op-amp is

$$A = 1 + \frac{R_f}{R_1}$$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$$

$$\frac{V_o}{V_{ref}} = 1 + \frac{R_f}{R_1}$$
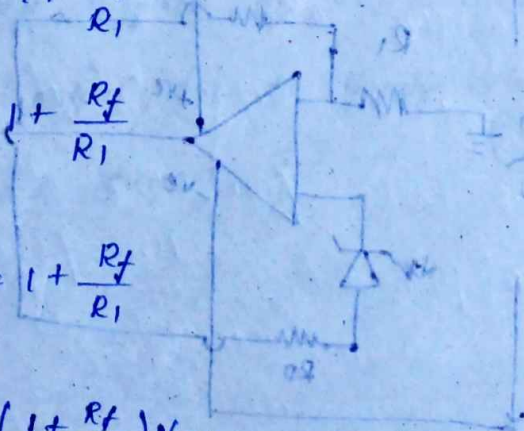
$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{ref}$$



If $V_{ref} = 5V$

$R_f = R_i$


$V_o = 2 V_{ref}$

$V_o = 10V$

If V_{ref} is fixed and $R_f = R_i$, the output voltage is fixed at $V_o = 2 V_{ref}$ that is the output voltage is fixed at 10 volts. and any variation in unregulated power supply +ve and -ve absorb in the op-amp and output is constant.

→ the output can be varying the R_i , R_f and V_{ref} remaining all cases is constant.

With Zener diode:-

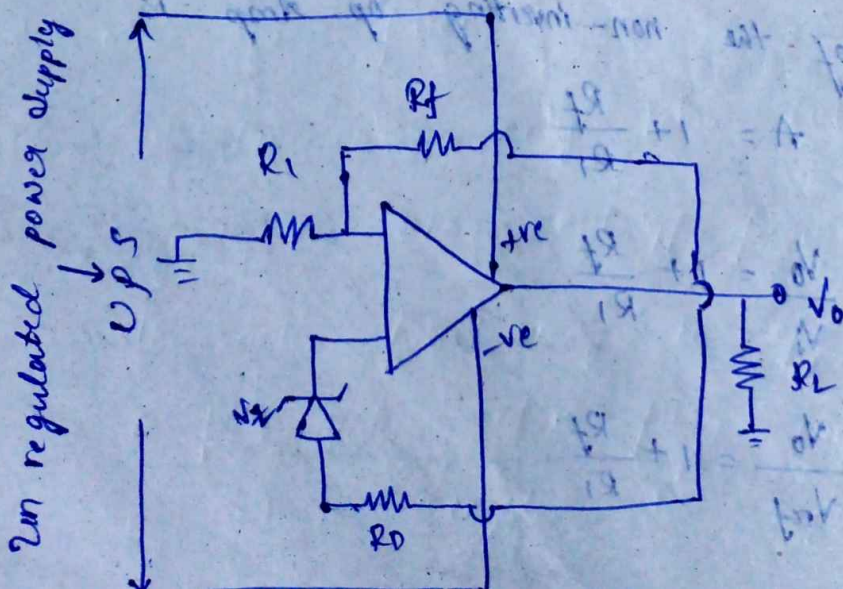

→ the above diagram shows the op-amp as regulated circuit with Zener diode.

→ Zener diode should be ^{made to} operate only in the break down region.

→ the value of the Zener voltage (V_Z) should be less than the output voltage.

$$V_Z < V_O$$

$$V_Z = 5V$$

$$R_f = R_1$$

$$V_O = 2V_Z$$

$$V_O = 10V$$

→ the Zener diode is properly loaded a given fixed voltage (V_Z) to the non-inverting terminal

→ hence, output voltage is fixed at $2V_Z$ by eliminating any variations in the output due to supply voltage

+ve and -ve and load current I_L

Active filters:- A frequency selective electric circuit that passes electrical signals of specified random frequencies and attenuates then signals of frequency outside the ~~bag~~ band is called as active filters.

→ filters may be called as active (or) passive according to the presence (or) absence of an active devices respectively.

→ RC active filters:- op-amp is used as an active device while resistance and capacitance are used as passive device.

Types of filters:-

i) Low pass filter

ii) High pass filter


iii) Band pass filter

↓ Low pass filter:-

→ It can allow only below cut-off frequency and reject the above cut-off frequency.

→ the active filters may be of different orders

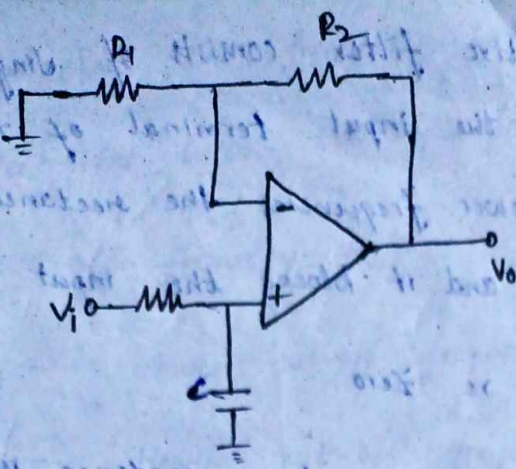→ A first order active filter consists of single RC Network connected to input terminal of the op-amp.




→ Capacitor reactance $X_c = \frac{1}{\omega c}$
 $X_c = \frac{1}{2\pi f c}$

→ At low frequency capacitor appears as a open.

→ As the frequency increases capacitor reactance is increases then decreases in the voltage input.

→ Here f_c be the value of the signal frequency at which the o/p decreases to 0.707 times its low frequency value



$$f_c = \frac{1}{2\pi R c}$$

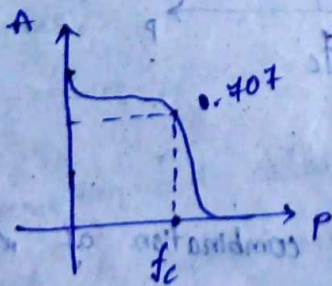

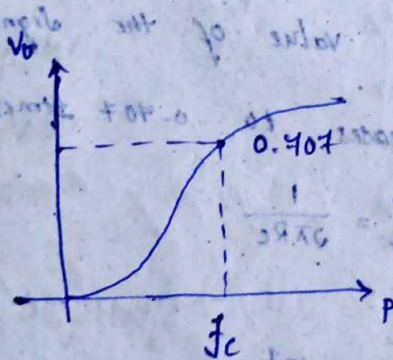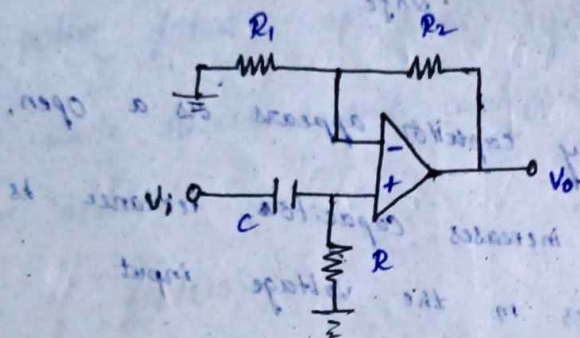(ii) High pass filter:-

→ It can allow only above cut-off frequency and reject the below cut-off frequency.

- A first order active filter consists of single Re Network connected to the input terminal of the op-amp.
- In this case at lower frequencies the reactance of capacitor is infinite and it blocks the input signal hence the output is zero.
- Increasing the frequency capacitive reactance is decreases and output is increases.





Band filter:-

- Band filter is the combination of low pass filter and high pass filter.
- It can allow only certain band of frequencies and ~~remain~~ reject the remaining band of the frequency.

→ It can allow the frequency between f_{c1} and f_{c2} and reject the below cut-off frequency f_{c1} and above cut-off frequency f_{c2}

f_{c1} → lower cut-off frequency

f_{c2} → higher cut-off frequency.

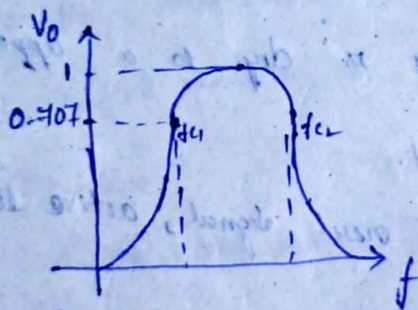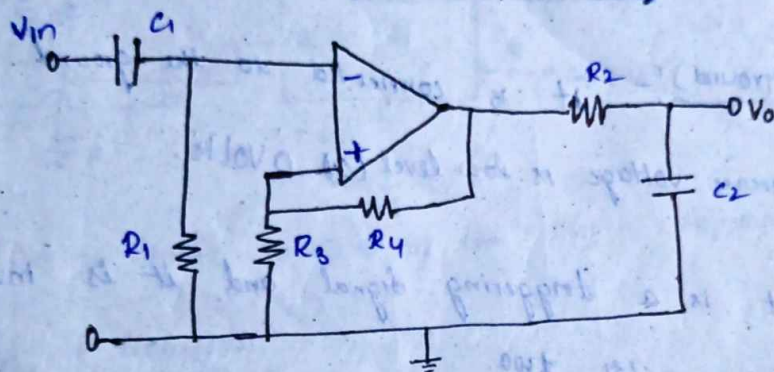

555-IC Timer:-

→ If ~~the~~ 555 timer is an integrated circuit used in

timer pulse generation and ~~other~~ oscillations applications.


→ It is used to provide the time delay.

→ It is an 8-pin IC developed by using C-MOS technology.

→ A 555 timer can be used to modulate the signals

and create accurate clock signals, create pulse with modulated signals.

Pin diagram of 555 IC:-

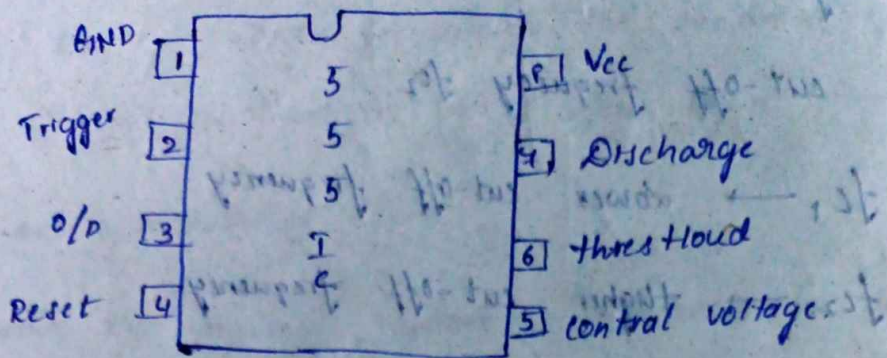

PIN I (Ground):- It is connected to the ground the ground reference voltage is low level (0) volts.

PIN II:- It is a triggering signal and it is inverting input of comparator two.

PIN III:- the output is dry to a approximately 0.707 below Vcc (on ground).

PIN IV:- It is a reset signal, active low signal (0)


PIN V:- provides control across to the internal voltage divider $\frac{2}{3}$ of Vcc

PIN VI:- (Threshold) It is a non-inverting input of comparator 1.

PIN VII (Discharge):- open collector output which may discharge a capacitor b/w intervals.

PIN VII (V_{CC}) It is a +ve supply voltage b/w the 3V & 15V depending upon the variants. Variations.

functional block diagram of 555 IC:-

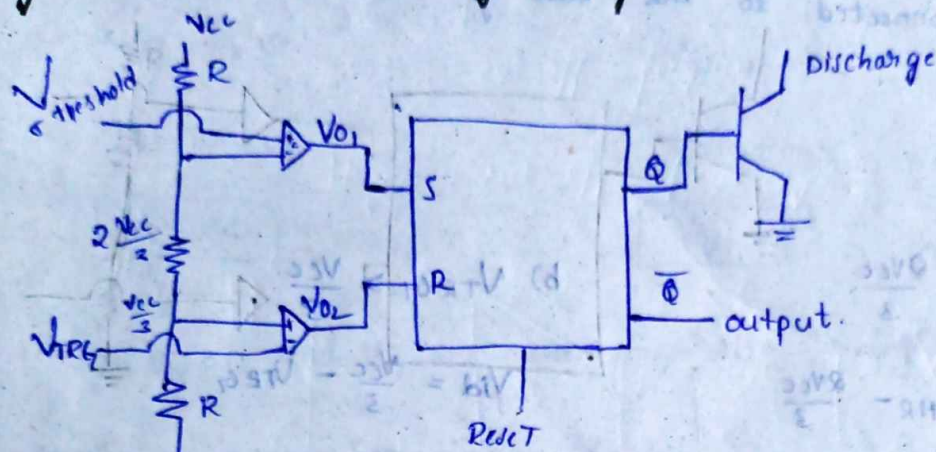

→ 555 IC timer consists of the two comparators, 1 SR-flip flop, 1 transistor.

→ the inputs to the comparator 1, is $V_{threshold}$ and $\frac{2V_{CC}}{3}$ and its output is V_{01} when it is connected to the input

to the SR flip-flop.

→ the inputs to the comparator $\frac{2V_{CC}}{3}$, V_{trig} and its output is V_{02} then it is connected to the input of

SR-flip flop.

S R Q Q

○

○

m.s

○

(Reset)

○

(Set)

IV

- the outputs of SR flipflop is ϕ and $\bar{\phi}$.
- the 555 timer I_C can be taken at $\bar{\phi}$.
- $\bar{\phi}$ is connected to the base of the transistor.

Working:-

Case ①:-

a) $V_{THR} > \frac{2V_{CC}}{3}$

$$V_{id} = V_{THR} - \frac{2V_{CC}}{3}$$

$$V_{id} \geq +ve$$

$$V_{O1} = +ve$$

$$V_{O1} = +ve$$

b) $V_{TRCH} > \frac{V_{CC}}{3}$

$$V_{id} = \frac{V_{CC}}{3} - V_{TRCH}$$

$$V_{id} = -ve$$

$$V_{O2} = -ve$$

$$V_{O2} = -ve$$

→ $V_{O1} = 1$, and $V_{O2} = 0$ then inputs to the SR flipflop

$$S = 1, R = 0$$

→ If $S = 1, R = 0$ then SR-flipflop is in "Set condition"

$$\text{that } \phi = 1 \text{ and } \bar{\phi} = 0$$

→ $\bar{\phi}$ is the 555 timer output that is Zero.

→ $\bar{\phi}$ is connected to the base of the transistor then

transistor is in saturation region. It will be acts a short circuit and ϕ is connected to the ground

they output is Zero. then capacitor is Zero.

Case 2

a) $V_{thR} < \frac{2V_{CC}}{3}$

$$V_{id} = V_{thR} - \frac{2V_{CC}}{3}$$

$$V_{id} = +ve$$

$$V_{01} = -ve$$

$$V_{01} = 0$$

b) $V_{thR} < \frac{V_{CC}}{3}$

$$V_{id} = \frac{V_{CC}}{3} - V_{thR}$$

$$V_{id} = +ve$$

$$V_{02} = +ve$$

$$V_{02} = 1$$

→ If $V_{01} = 0$ and $V_{02} = 1$ then are the inputs of SR-flip flop

then its outputs are $Q = 0$, $\bar{Q} = 1$

→ the 555 timer IC output is \bar{Q} that is 1.

→ If $Q = 0$. It is connected to the base of the transistor

then transistor is in cut-off region and it acts as an open circuit. A voltage will be existing at the open circuited terminal. then output = 1.

Applications

- Temperature, measurement and control devices
- Traffic signal light control circuits.
- It is used to make an alarm circuit.
- used in digital counter circuit.
- Pulse generation, time delay generation, voltage controlled oscillations, frequency division applications.
- All electronic projects.


Square wave generator

It is also called as Schmitt trigger.

→ If positive feedback is added to the comparator circuit then it is set to be Schmitt trigger (or)

Square wave generator.

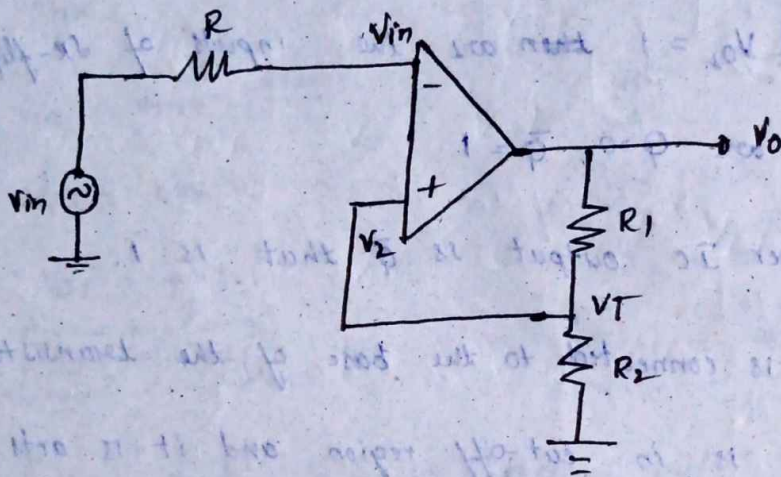→ It is also called regenerative comparator.



→ Some position of the output will go back to the input.

Now, voltage divider rule at $V_T = \frac{V_O R_2}{R_1 + R_2}$

Case-1

$$V_{in} > V_T$$

$$V_{id} = V_T - V_{in}$$

$$V_{id} < -V_e$$

$$V_O = -V_e$$

$$V_O = -V_{sat}$$

(case II) :-

$$V_{in} < V_T \quad \text{---} \quad 900V = 10V$$

$$V_{id} = \frac{V_T + V_{in}}{1 + 1.9} = \frac{10 + 9}{2.9} = 4V$$

$$V_{id} = +ve$$

$$V_o = +ve \quad \frac{10}{1.9} = 4V$$

$$V_o = +V_{sat} \quad \text{---} \quad \text{threshold}$$

→ If $V_o = +V_{sat}$ then threshold voltage is called as upper threshold potential.

$$V_o = +V_{sat}$$

$$V_T = \frac{R_2}{R_1 + R_2} (+V_{sat})$$

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{sat})$$

$$(2-3-8)$$

→ If $V_o = -V_{sat}$ then threshold voltage is called as lower threshold potential.

$$V_o = -V_{sat}$$

$$V_T = \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$

→ the difference between the upper threshold potential and lower threshold potential is called as hysteresis.

$$V_H = V_{UTP} - V_{LTP} \quad V > 0V$$

$$V_H = \frac{R_2}{R_1 + R_2} (+V_{sat}) + \frac{R_1}{R_1 + R_2} (-V_{sat})$$

$$V_H = \frac{R_2}{R_1 + R_2} (2V_{sat})$$

(i) $V_{in} > V_{UTP}$; $V_o = -V_{sat}$

(ii) $V_{in} < V_{UTP}$; $V_o = +V_{sat}$

(iii) $V_{in} > V_{LTP}$; $V_o = +V_{sat}$

(iv) $V_{in} < V_{LTP}$; $V_o = -V_{sat}$

Example :- (iii)

$V_{in} = -5$ and $V_{LTP} = -3$

Now $V_H = V_{LTP} - V_{in}$
 $= -3 - (-5)$

