

SINUSOIDAL ALTERNATING WAVE FORMS

Current: Flow of the charge carriers per unit time is called as current.

$$I = \frac{Q}{t} = \frac{\text{charge}}{\text{Time}}$$


Units of current is amperes (or) Coulombs/sec

- Both positive & negative of electrons is known as charge units of charge 'Coulombs'.

Voltage: Potential difference between two points in a conductive loop is called as voltage; also referred as amplitude.

- To move the electrons from one position to another position in a semiconductor material some pressure is applied across the electrons is referred as a potential.

Units of voltage is 'volt'

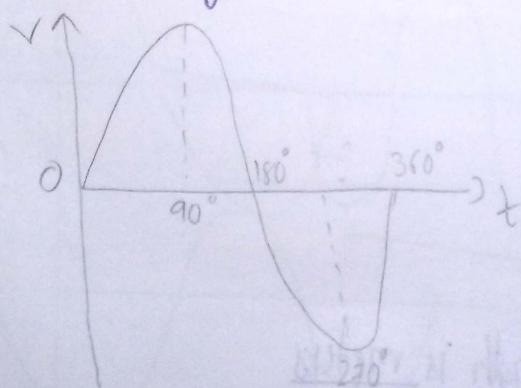

Time period: Time taken for one complete cycle or oscillation is called as time period.

- Units of time period is seconds.

Frequency: No. of cycles or oscillations per second is called as frequency.

Units of frequency is "hertz" (Hz)


- Time period and frequency are inversely proportional to each other.

$$T = \frac{1}{f}$$

Amplitude: Peak to peak value of the sine wave is called as amplitude.

- Units of amplitude is 'volts'.

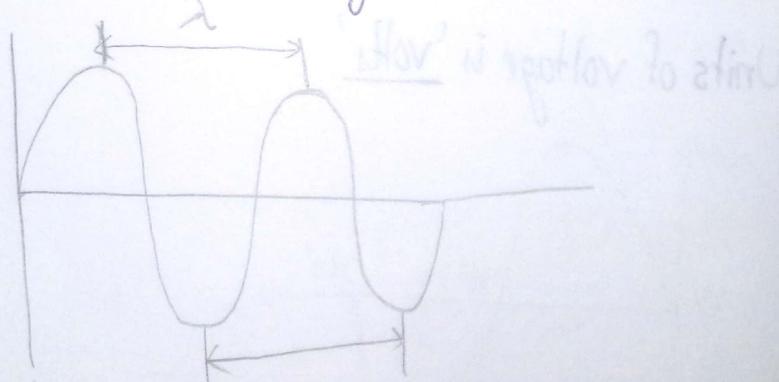Wave length: distance between the two peak points of the sine wave (or) two depth points of the sine wave is called wavelength.



Units of wavelength is meters

Phase Difference:

- If two sine waves are in same phase are inphase then phase difference α is zero.
- If two sine waves are in out of phase the phase difference is leading (or) lagging depends upon the condition.

Sinusoidal format for voltage:

- The standard equation of sine wave for a voltage is

$$V(t) = V_m \sin \omega t$$


$V(t)$ = instantaneous value

V_m = maximum value (or) peak value

ω = angular frequency

$$\omega = 2\pi f \text{ (or) } \frac{2\pi}{T}$$

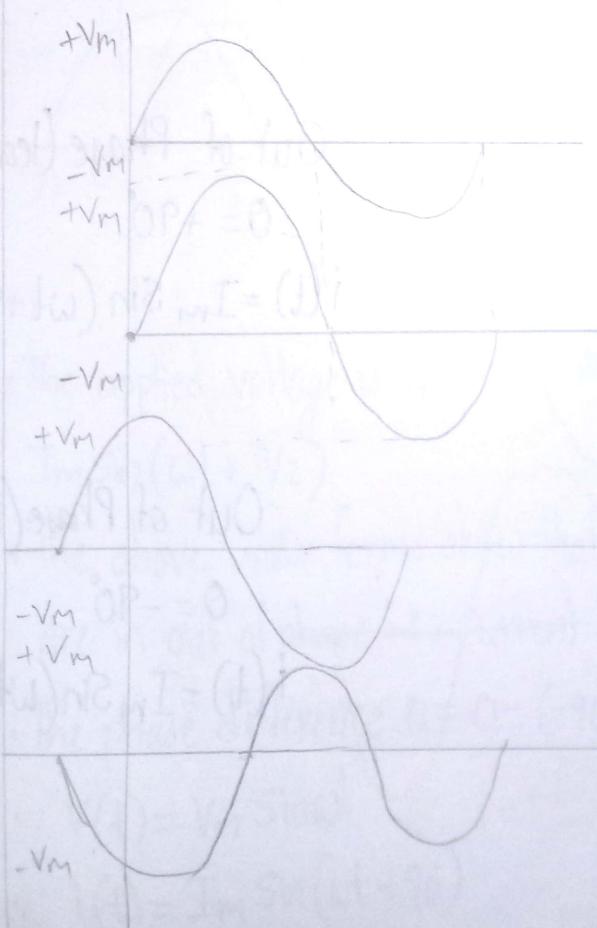Comparing different waves with general eqn of Sine wave



$$V(t) = V_m \sin(\omega t + \theta)$$

In Phase, $\theta = 0$

$$V(t) = V_m \sin \omega t$$

Out of Phase

$$\theta = +90^\circ; \text{(leading)}$$

$$V(t) = V_m \sin(\omega t + 90^\circ)$$

Out of Phase

$$\theta = -90^\circ; \text{(lagging)}$$

$$V(t) = V_m \sin(\omega t - 90^\circ)$$

Sinusoidal format for current:

The standard eqn of sine wave of current is

$$i(t) = I_m \sin(\omega t + \theta)$$


$i(t) \rightarrow$ instantaneous current

$I_m \rightarrow$ maximum current

$\omega \rightarrow$ angular frequency $\omega = 2\pi f (or) \frac{2\pi}{T}$

$\theta \rightarrow$ phase difference

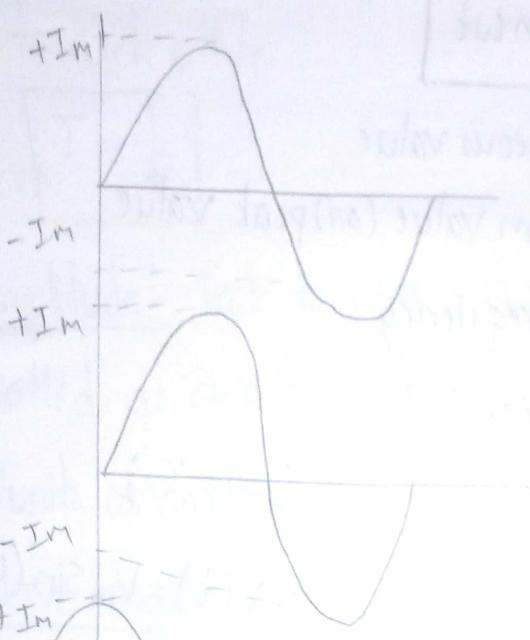
Comparing general sine wave with different waves



$$i(t) = I_m \sin(\omega t + \theta)$$

In phase, $\theta = 0$


$$i(t) = I_m \sin \omega t$$

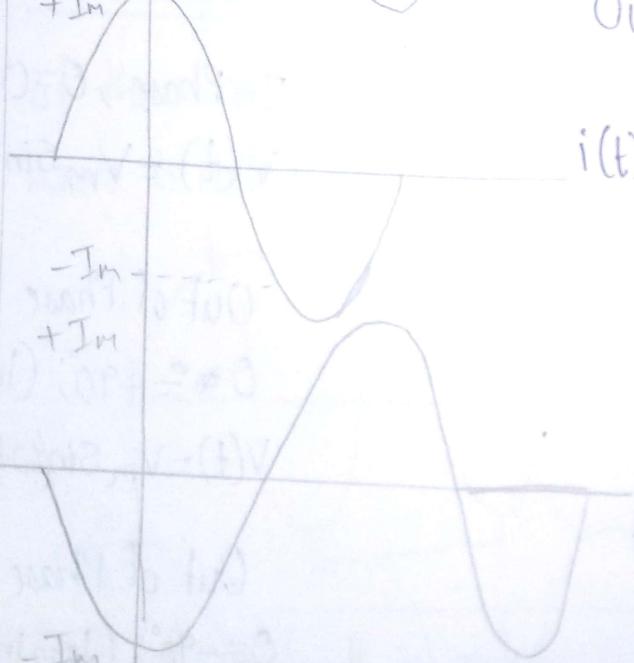

Out of Phase (leading)

$$\theta = +90^\circ$$

$$i(t) = I_m \sin(\omega t + 90^\circ)$$

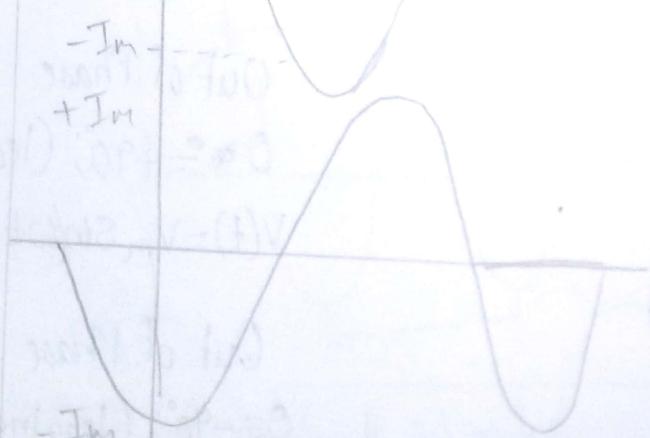


Out of Phase (lagging)

$$\theta = -90^\circ$$


$$i(t) = I_m \sin(\omega t - 90^\circ)$$

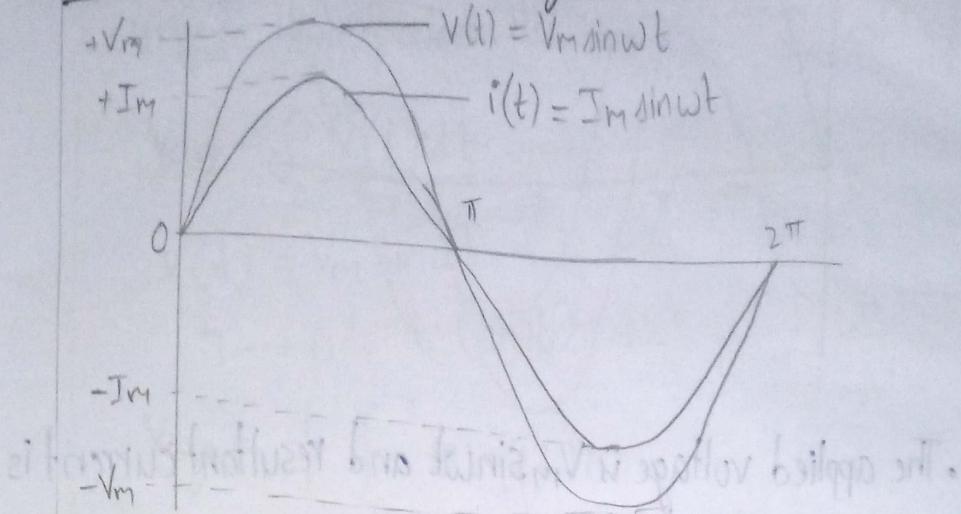Phase relation between voltage & current:




- The applied voltage is $V_m \sin \omega t$ and resultant current is $I_m \sin \omega t$.
- The above wave form show the voltage and current are in same phase (or) inphase i.e., phase difference is zero ($\theta = 0$)
 $v(t) = V_m \sin \omega t$

$$i(t) = I_m \sin \omega t$$

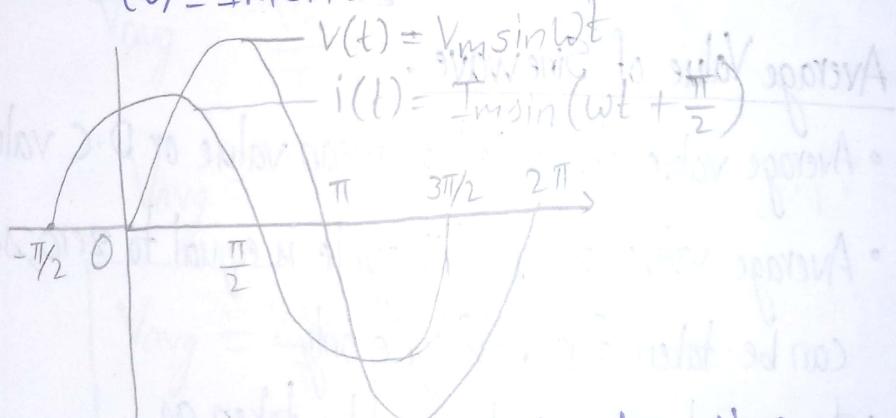

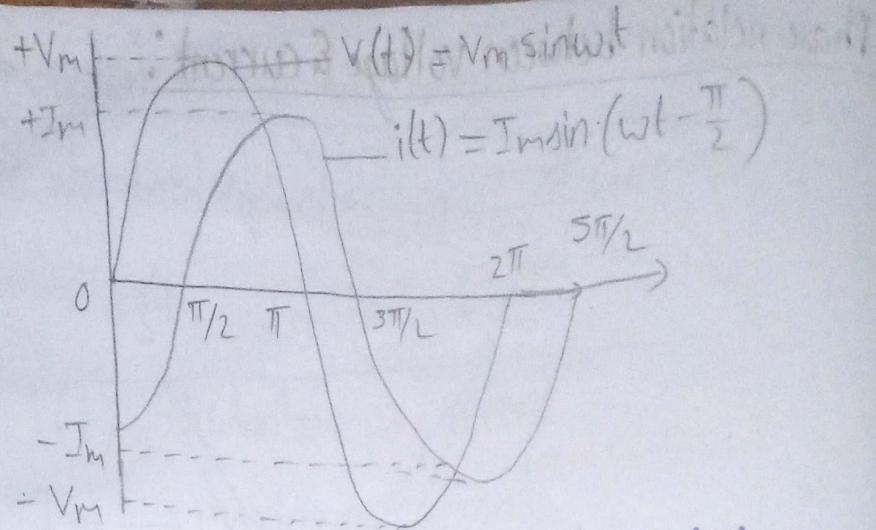- The applied voltage is $V_m \sin \omega t$ and resultant current is $I_m \sin(\omega t + \pi/2)$.
- The above wave forms show that voltage and current are in out of phase i.e., current leads voltage by 90° .
- The phase difference $\theta = 0 - (-90^\circ) = 90^\circ$
- $v(t) = V_m \sin \omega t$
- $i(t) = I_m \sin(\omega t + 90^\circ)$



- The applied voltage is $V_m \sin wt$ and resultant current is $I_m \sin(wt - \pi/2)$.

- The above wave form shows the voltage & current are in out of phase i.e., currents lags voltage by 90° .

- The phase difference $\theta = 0 - 90^\circ = -90^\circ$


$$V(t) = V_m \sin wt$$

$$i(t) = I_m \sin(wt - \frac{\pi}{2})$$

Average Value of Sine wave:

- Average value also called as mean value or D.C value.
- Average value of one full cycle is equal to zero, so it can be taken for half cycle only.
- In general average value can be taken as
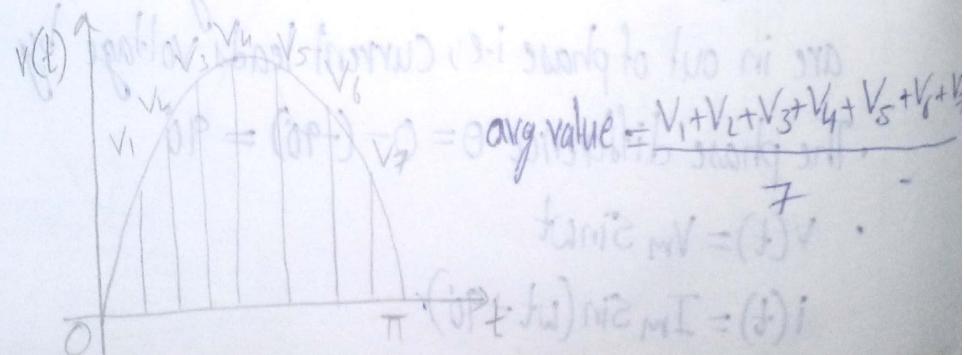
$$\text{Avg. value} = \frac{\text{sum of observations}}{\text{no. of observations}}$$



- Mathematically it can be defined as ratio of area of the curve to time period

$$V_{avg} = \frac{\int_0^T v(t) dt}{T}$$

$$v(t) = V_m \sin \omega t$$

$T \rightarrow 0$ to π (limits)

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t dt$$

$$V_{avg} = \frac{V_m}{\pi} \left[\int_0^{\pi} (\sin \omega t) dt \right]$$

$$V_{avg} = \frac{V_m}{\pi} \left[(-\cos \omega t) \Big|_0^{\pi} \right]$$

$$V_{avg} = \frac{V_m}{\pi} \left[-(\cos \pi) - (\cos 0) \right] = \frac{V_m}{\pi} [1 - 1] = 0$$

$$V_{avg} = \frac{V_m}{\pi} \left[-(-1) - (-1) \right] = \frac{2V_m}{\pi}$$

$$\boxed{V_{avg} = \frac{2V_m}{\pi}}$$

- Average value of sine wave is equal to 0.636 times of its maximum value


$$\boxed{V_{avg} = 0.636 V_m}$$

$$\frac{16}{\pi} \left[\frac{1}{2} \sin(16\pi) - \frac{1}{2} \right] \cdot \frac{100}{75} =$$

RMS value of Sine Value:

RMS means Root Mean Square value it can also called as effective value.

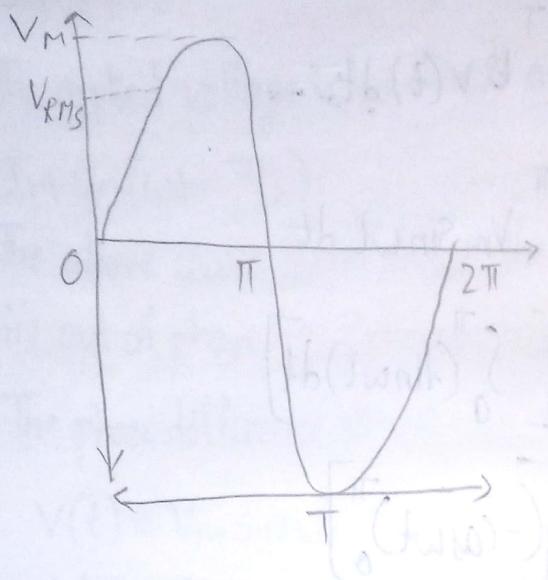- It can be calculated to entire full cycle.
- It is used to measure the heating effect of the wave.



$$V_{RMS} = \sqrt{(V_{avg})^2}$$

$$V_{RMS}^2 = (V_{avg})^2$$

$$= \frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 dt$$

$$= \frac{V_m^2}{2\pi} \int_0^{2\pi} (\sin^2 \omega t) dt$$

$$= \frac{V_m^2}{2\pi} \int_0^{2\pi} \left[\frac{1 - \cos 2\omega t}{2} \right] dt$$

$$= \frac{V_m^2}{4\pi} \int_0^{2\pi} (1 - \cos 2\omega t) dt$$

$$= \frac{V_m^2}{4\pi} \int_0^{2\pi} 1 dt - \int_0^{2\pi} \cos 2\omega t dt$$

$$= \frac{V_m^2}{4\pi} \left[t \right]_0^{2\pi} - \left[\frac{\sin 2\omega t}{2\omega} \right]_0^{2\pi}$$

$$V_{RMS}^2 = \frac{V_m^2}{4\pi} \left[(2\pi - 0) - \left(\frac{\sin 4\pi\omega}{2\omega} - \frac{\sin 0\omega}{2\omega} \right) \right]$$

$$V_{RMS}^2 = \frac{V_m^2}{4\pi} \left[(2\pi) - [0 - 0] \right] \quad \begin{matrix} \text{E: } \sin n\pi = 0 \\ \text{dih } 0^\circ = 0 \end{matrix}$$

$$V_{RMS}^2 = \frac{V_m^2}{2 \cdot 4\pi} (2\pi)$$

$$V_{RMS}^2 = \frac{V_m^2}{2} \Rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$$

R.M.S value of the sine wave is equal to the 0.707 times of its maximum value

$$V_{RMS} = \frac{V_m}{1.414} \Rightarrow V_{RMS} = 0.707 V_m$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}} \Rightarrow I_{RMS} = 0.707 I_m$$

AC response of the pure resistor:


- The AC voltage is applied to a pure resistor circuit then its applied voltage $V = V_m \sin \omega t$

From Ohm's law, $V = IR \quad \text{--- } ①$

applied voltage $V = V_m \sin \omega t \quad \text{--- } ②$

$$V_m \sin \omega t = IR$$

$$V = V_m \sin \omega t$$

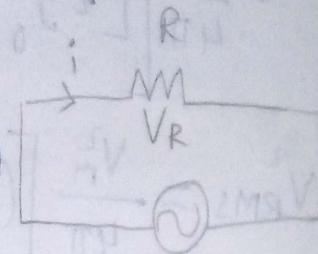

$$I = \frac{V_m \sin \omega t}{R}$$

$$I = \frac{V_m}{R} \sin \omega t$$

$V = \text{voltage across resistor}$


$$\left(\frac{V_m}{R}\right) \frac{V}{\text{ms}} = \frac{V}{\text{ms}}$$

$$I_m = \frac{V_m}{R}$$


$$I = I_m \sin \omega t$$

The applied voltage $V = V_m \sin \omega t$ and its resultant current is $I = I_m \sin \omega t$.

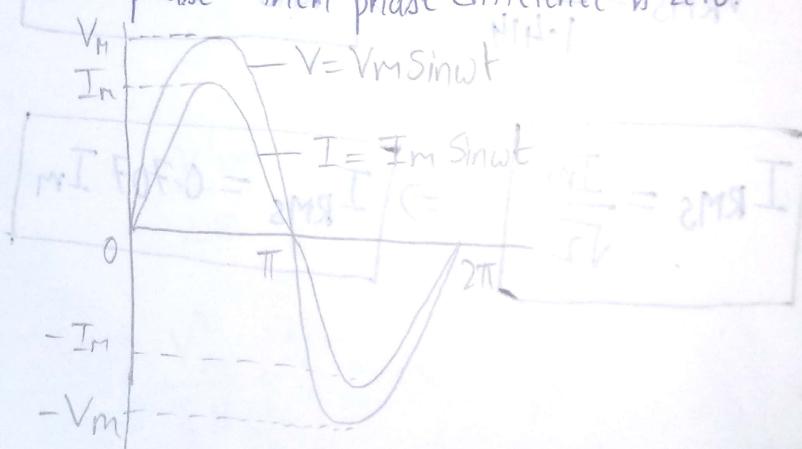- The applied voltage & resultant current are "inphase" or "same phase" then phase difference is zero.



Phasor Diagram:

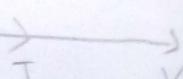

I & V are in same phase


AC response of the pure capacitor:

The AC voltage is applied to a pure capacitor or pure circuit then its applied voltage is $V = V_m \sin \omega t$

The charge of capacitor is $Q = CV$

$$\text{current } i = \frac{Q}{t}$$

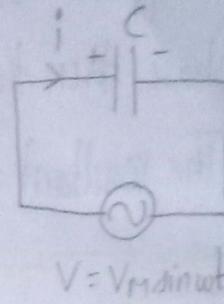differentiate the charge of capacitor w.r.t. 't'



$$\frac{dQ}{dt} = \frac{d}{dt}(CV)$$

$$i = C \frac{dV}{dt}$$

$$i = C \frac{d}{dt}(V_m \sin \omega t)$$

$$i = V_m C \frac{d}{dt}(\sin \omega t)$$

$$i = V_m C (\cos \omega t) \omega$$

$$i = V_m C \omega (\cos \omega t)$$

$$i = \frac{V_m}{X_C} (\cos \omega t)$$

$$i = I_m \cos \omega t$$

$$i = \boxed{I_m = \frac{V_m}{X_C}}$$

$$i = I_m \cos \omega t$$

$$i = I_m \sin(90^\circ + \omega t)$$

$$i = I_m \sin(\omega t + 90^\circ)$$

$$X_C = \frac{1}{2\pi f C}$$


$$X_C = \frac{1}{\omega C}$$

X_C = capacitive reactance


$$\boxed{V = V_m}$$

The applied voltage $V = V_m \sin \omega t$ and its resultant current $i = I_m \sin(\omega t + \frac{\pi}{2})$

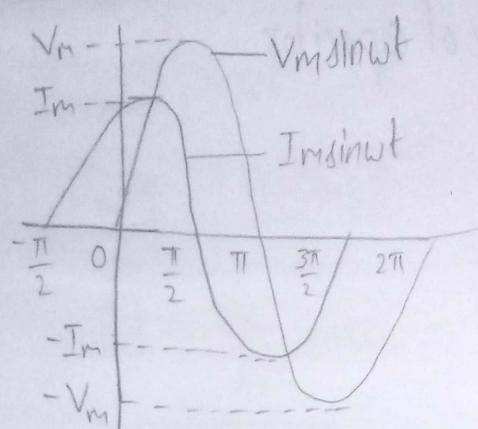- The applied voltage and resultant current are in out of phase then the phase difference is 90° (leading)
- The resultant current leads applied voltage by 90° .



Phasor diagram

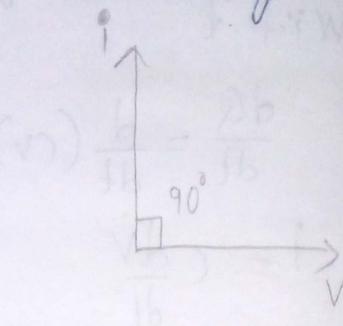


AC response of the pure inductor:

- The AC voltage is applied to the pure inductor circuit then its applied voltage is $V = V_m \sin \omega t$

The applied voltage $\Rightarrow V = V_m \sin \omega t$

Voltage across inductor is

$$V_L = L \cdot \frac{di}{dt}$$

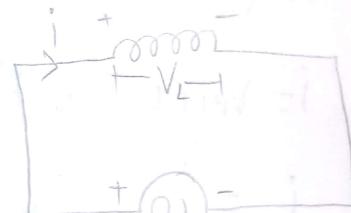

$$V_{\text{ind}} = V_m \sin \omega t$$

apply KVL to above circuit, $V_L = \text{Voltage across inductor}$

$$V(t) - V_L = 0$$

$$V = V_L$$



$$\int \omega \cos \omega t = 1$$

$$(j\omega + jP) \cos \omega t = i$$

$$(jP + j\omega) \cos \omega t = i$$

$$V = V_m \sin(\omega t)$$

$$\frac{di}{dt} = \frac{V_m \sin(\omega t)}{L}$$

$$\frac{di}{dt} = \frac{V_m \sin(\omega t)}{L}$$

Apply \int on both sides

$$\int \frac{di}{dt} dt = \frac{V_m}{L} \int \sin(\omega t) dt$$

$$i = \frac{V_m}{L} \int \sin(\omega t) dt$$

$$i = \frac{V_m}{L} \left[-\frac{\cos(\omega t)}{\omega} \right]$$

$$i = \frac{V_m}{\omega L} (-\cos(\omega t))$$

$$i = \frac{V_m}{X_L} (-\cos(\omega t))$$

$$I_m = \frac{V_m}{X_L}$$

$$i = I_m (-\cos(\omega t))$$

$$i = I_m (-\sin(90 - \omega t))$$


$$i = I_m \sin(\omega t - 90^\circ)$$

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

The applied voltage $V = V_m \sin(\omega t)$ and resultant current

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

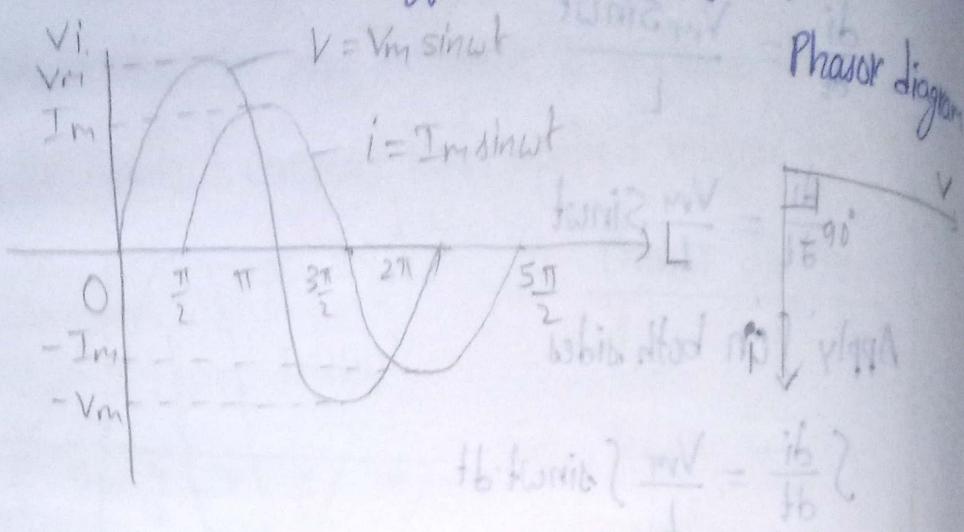- The applied voltage & resultant current are in out of phase, then phase difference = -90°
- The resultant current lags applied voltage by 90° .



Pb: An alternating current is represented by $i = 220 \sin(157t + \frac{\pi}{2})$. Calculate the (a) frequency (b) Time period (c) peak value (d) Mean value (e) RMS value.

$$i = 220 \sin\left(157 + \frac{\pi}{2}\right) \quad (\text{f}, \omega) \rightarrow \frac{mV}{i} = i$$

$$I_m = 220 \quad \omega = 157 \quad \theta = \frac{\pi}{2} \quad (\text{f}, \omega) \rightarrow \frac{mV}{i} = i$$

$$(a) \omega = 2\pi f$$

$$157 = 2\pi f$$

$$f = \frac{157}{2 \times \frac{22}{7}} = 24.97 \approx 25 \text{ Hz} \quad (\text{f} = 25 \text{ Hz})$$

$$(b) \text{Time period} \Rightarrow f = \frac{1}{T} \quad (\text{f} = \frac{1}{T}) \rightarrow \frac{mV}{i} = i$$

$$\Rightarrow T = \frac{1}{f} \quad (\frac{1}{f} = T) \rightarrow \frac{mV}{i} = i$$

From this formula $\frac{1}{25}$ and $mV = V$ gives $T = 0.04 \text{ sec}$

$$T = 0.04 \text{ sec}$$

$$(\frac{1}{f} = T) \rightarrow \frac{mV}{i} = i$$

(c) peak value (I_m)

$$I_m = 220$$

(d) Mean value

$$I_{avg} = \frac{2I_m}{\pi} = \frac{2 \times 220}{\pi} = \frac{440}{\pi} = 140.12$$

$$I_{avg} = 140.12$$

(e) R.M.S value

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

$$I_{RMS} = \frac{220}{1.414}$$

$$I_{RMS} = 155.58 \text{ amp}$$

A sinusoidal wave form is given by $I = 10 \sin(6284t + 10^\circ)$

find its (a) peak value (b) R.M.S value (c) frequency

(d) Time period.

Sol: (a) peak value $\Rightarrow 10$

$$I = 10 \sin(6284t + 10^\circ)$$

$$I = I_m \sin(\omega t + \theta)$$

$$I_m = 10, \omega = 6284, \theta = 10^\circ$$

(a) peak value (I_m) $= 10$

(b) R.M.S value

$$I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{10}{1.414} = 7.07 \text{ amp}$$

(c) Frequency

$$\omega = 6284$$

$$2\pi f = 6284$$

$$f = \frac{6284}{2\pi} = \frac{6284}{6.28} = 1000 \text{ Hz} = 1 \text{ kHz}$$

(d) Time period

$$f = \frac{1}{T} \Rightarrow f = \frac{1}{1 \times 10^3} = 1 \times 10^{-3} \text{ ms}$$

- An alternating current of frequency 50 Hz has the maximum value of 100 amp. Write down the equation for its instantaneous value.

Sol:

$$f = 50 \text{ Hz}$$

$$I_m = 100 \text{ Amp}$$

$$i = I_m \sin(\omega t + \theta)$$

$$\theta = 0$$

$$\omega = 2\pi f$$

$$\omega = 2\pi \times 50 = 100\pi$$

$$\omega = 100 \times 3.14 = 314$$

$$\therefore i = 100 \sin 314t$$

- A sinusoidal voltage $V = 200 \sin 314t$ is applied to a resistor of 10Ω resistance. Calculate the (a) R.M.S value of the voltage (b) R.M.S value of the current (c) power dissipated as heat (in Watts)

Sol: Given $V = 200 \sin 314t$

$$\text{Here } V_m = 200 \quad R = 10\Omega \quad = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 200\sqrt{2} \text{ V}$$

(i) R.M.S value of voltage

$$V_{RMS} = \frac{Vm}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.4 \text{ Volts}$$

(ii) R.M.S value of current

$$I_{RMS} = I_m = \frac{Vm}{R} = \frac{200}{10} = 20$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.14 \text{ amp}$$

(iii) Power dissipated

$$P = V_{RMS} \times I_{RMS} = 141.4 \times 14.14 = 1999.396 = 2000 \text{ watts}$$

$$\boxed{P=VI}$$

P = power
V = voltage
I = current

An alternating current is given by $I = 141.4 \sin 314t$

Find the (a) Maximum value of current (b) frequency
(c) time period

∴ $I = I_m \sin(\omega t + \theta)$

$$I = 141.4 \sin 314t$$

$$\therefore I_m = 141.4 \quad \omega = 314 \quad \theta = 0^\circ$$

(a) Maximum value of current $I_m = 141.4$

(b) Frequency

$$\omega = 2\pi f \Rightarrow f = \frac{\omega}{2\pi} = \frac{314}{2 \times 3.14} = \frac{314}{62.8} = 50 \text{ Hz}$$

(c) Time Period

$$T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec}$$

- Find the peak value, average value and RMS value of an alternating current represented by $I = 28.4 \sin(628t)$

(i) $I = I_m \sin(\omega t + \phi)$

$$I_p = 28.4 \sin(628t)$$

$$I_m = 28.4 \quad \omega = 628$$

(i) Peak value = $I_m = 28.4$

(ii) Average value

$$I_{avg} = \frac{2I_m}{\pi} = \frac{2 \times 28.4}{3.14} = 18 \text{ Amp}$$

(iii) R.M.S value

$$I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{28.4}{1.414} = 20 \text{ amp}$$

- If AC mains supply is 220 Volts then find the average power during a positive half cycle?

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

$$V_m = V_{RMS} \times \sqrt{2} = 220 \times 1.414 = 311 \text{ Amp Volts}$$

$$V_{avg} = \frac{2V_m}{\pi} = \frac{2 \times 311}{3.14} = 198 \text{ Amp Volts}$$



$$P_{avg} = \frac{V_m^2}{R} = \frac{311^2}{100} = \frac{96721}{100} = 967.21 \text{ Watts}$$

$$\frac{T}{4} = \frac{1}{20} = 0.05 \text{ sec}$$

Difference b/w AC and DC:

A.C D.C

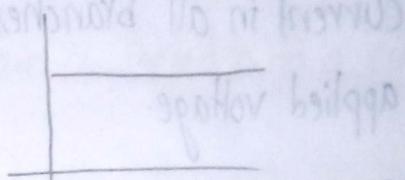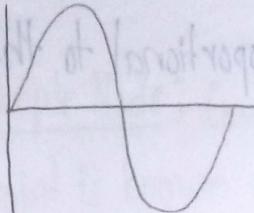- A.C means alternating current.
- It is a signal which changes magnitude and polarity.
- Frequency is 50 Hz
- It is a bidirectional.
- D.C means direct current.
- It is a signal which changes magnitude but not polarity.
- Frequency is 0 Hz.
- It is a unidirectional.



- It provides long distance transmission.
- It is produced from the power stations.
- Distribution efficiency is high.
- Power consumption is low.
- Power factor is lies between 0 to 1.
- Use of transformer is possible.
- AC motors, domestic and industrial supply applications.
- It provides short distance transmission.
- It is produced by battery.
- Distribution efficiency is low.
- Power consumption is high.
- Power factor is '1'
- DC machines, HBV DC system applications.