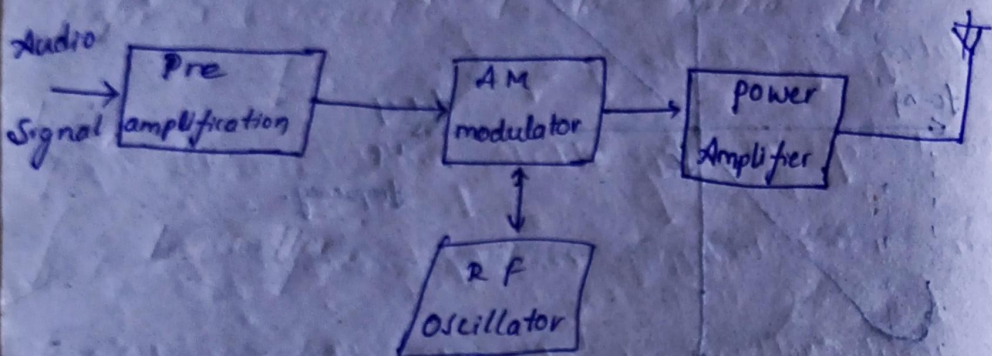


## UNIT-V

### Radio broadcasting and reception.

#### Am Transmitter:



→ the above figure shows the block diagram of the Am transmitter.

→ the Transmitter can transmit the Am signals are known as Am Transmitter.

→ these transmitter are used in medium wave and short wave frequency bands for Am Broad cast.

→ the medium wave as frequency b/w the

→ the consists of the different blocks

1) Pre amplifier, Am modulator, RF oscillator, power Amplifier.



Pre amplifier:- the input to the pre amplifier is audio signal that is low frequency signal. the strength of the signal ~~to~~ can be increase pre amplifier then its output amplified audio signal.

→ the output of the pre amplifier is connected to the Am modulator.

RF oscillator:-

→ In radio frequency oscillator the high frequency carrier wave is generated by using crystal control oscillator.

→ the output of the RF oscillator is connected to the Am modulator.

Am modulator:-

→ the inputs to the Am modulator is modulating the Af signal and Rf signal are mixed to produce the Amplitude modulated wave.

→ the output of amplitude modulator is connected to the power amplifier.




## power Amplifier:-

→ It is used to increase the power level of the amplitude modulated wave and output of power amplifier is connected to the antenna for

Transmission.

## fm transmitter:-

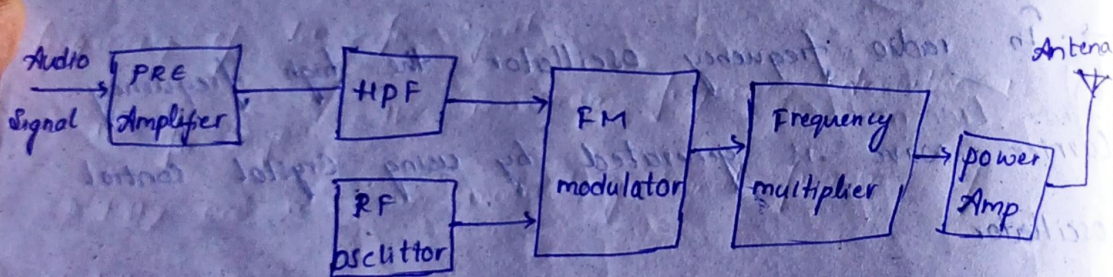

→ frequency modulation method is used in fm transmitter.

→ In fm frequency of the carrier signal is varied in accordance with amplitude of the modulating signal keeping its amplitude is constant.

→ the transmitters find application in radio, TV audio broadcasting and police wireless communication.

→ the frequency band extends from 88 - 108 MHz

→ the fm transmitter consists of the different block



Pre Amplifier, High pass filter, RF oscillator, Frequency modulator,  
frequency multiplier, power Amplifier.

### Pre Amplifier:-

→ the function of the pre amplifier is increase the strength of audio signal and it provides amplified output to the high pass filter.

### High pass filter:-

→ It allows only high frequency components and reject the low frequency components.

→ In this section high pass filter is used as pre-ambasis network by using high pass filter we can reduce the noise of the audio signal and improve the signal to noise ratio of the audio signal.

### RF oscillator:-

→ By using radio frequency oscillator we can generate the ~~frega~~ carrier signal.

→ It is a high frequency carrier signal.



frequency modulator:-  
→ the inputs to the frequency modulator is amplified audio signal and carrier signal.

→ By using direct method or indirect method we can generate the fm wave.

frequency multiplier:-

→ By using frequency multiplier we can increase the frequency of the fm signal.

→ In fm signal the maximum frequency deviation is  $\pm 75 \text{ kHz}$  and maximum modulating signal frequency of  $15 \text{ kHz}$ .

power Amplifier:-

→ the power of the carrier signal is then amplified in the power amplifier stage that is it can provides the required audio frequency power.

→ the output of the power Amplifier is connected to the Antenna Transmission.



# Radio Receivers

→ the primary requirement of the communication receivers is should have the ability to select the desired signal from among a no. of signals present and it provides sufficient amplification to recover the modulating signal.

→ Receivers perform the following functions:

- 1) Collect the electro magnetic waves by transmitter.
- 2) ~~desire~~ Select the desire signal and reject all other undesired signal.
- 3) Amplify the selected modulated signal.
- 4) detect the modulating signal from the modulated signal
- 5) Amplify the modulating signal operate the loud speaker.

Parameters of receiver:-

- 1) Sensitivity
- 2) Selectivity
- 3) Fidelity.