

# Unit-2 Boolean algebra and Theorems

$$B \cdot A = \overline{B} + A \quad (11)$$

postulates	a	b
postulate-2	$A+0=A$ <small><math>1+0=1</math> <math>0+0=0</math></small>	$A \cdot 1=A$ <small><math>1 \cdot 1=1</math> <math>0 \cdot 1=0</math></small>
postulate-3 (commutative law)	$A+B=B+A$	$AB=BA$
postulate-4 (Distributive law)	$A \cdot (B+C) = A \cdot B + A \cdot C$	$A+(B \cdot C) = (A+B) \cdot (A+C)$ <small>A, B, C Variable</small>
postulate-5	$A+\overline{A}=1$ <small><math>A=0 \quad \overline{A}=1 \quad 0+1=1</math></small>	$A \cdot \overline{A}=0$ <small><math>A=1 \quad \overline{A}=0 \quad 1 \cdot 0=0</math></small> <small>A, <math>\overline{A}</math> - Complement Non-complement</small>
Theorems	(a)	(b)
Theorem 1	$A+A=A$ <small><math>0+0=0</math> <math>1+1=1</math></small>	$A \cdot A=A$ <small><math>0 \cdot 0=0</math> <math>1 \cdot 1=1</math></small>
Theorem 2	$A+1=1$ <small><math>0+1=1</math> <math>1+1=1</math></small>	$A \cdot 0=0$ <small><math>0 \cdot 0=0</math> <math>1 \cdot 0=0</math></small>
Theorem 3	$\overline{\overline{A}} = A$	
Theorem 4	$A+AB=A$	$A(A+B)=A$
Theorem 5	$A+\overline{A}B=A+B$	$A(\overline{A}+B)=AB$
Theorem 6	$A+(B+C)=(A+B)+C$	$A(BC)=(AB)C$

denotation of Complement form is called Literal

## De-morgan's (law) (or) Theorem

$$1) \overline{AB} = \overline{A} + \overline{B}$$

The Complement of the product is equal's to Sum of the Complements

Truth Table :

A	B	$\overline{A}$	$\overline{B}$	AB	$\overline{AB}$	$\overline{A} + \overline{B}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0


(ii)  $\overline{A+B} = \overline{A} \cdot \overline{B}$   
 Complement of a Sum is equal to product of the Complement

A	B	$\overline{A}$	$\overline{B}$	$A+B$	$\overline{A+B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

Logic gates - Basic element of digital System

- AND, OR, NOT
- NAND, NOR
- EX-OR, EX-NOR

AND gate

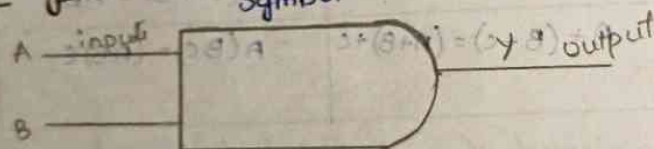

Boolean expression  $Y = A \cdot B$

Truth table:- one input is low then the output is low

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

OR gate




Boolean expression =  $Y = A + B$

Truth table :- one input is high then the output is high

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

## NOT Gate

Symbol :-

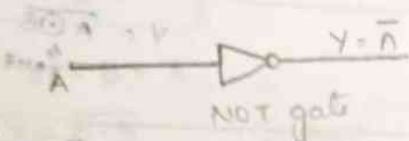


Truth table :-

A	$Y = \bar{A}$
0	1
1	0

## NAND gate

NAND = AND + NOT

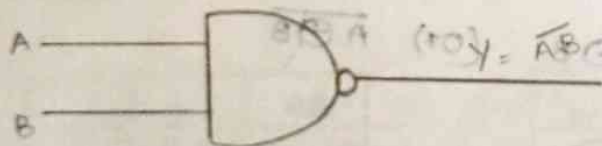

if any one input is low then output is high

A	B	$Y = \bar{A} \cdot \bar{B}$
0	0	1
0	1	0
1	0	0
1	1	0

## NOR gate


NOR = OR + NOT





A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

## Exclusive-OR gate

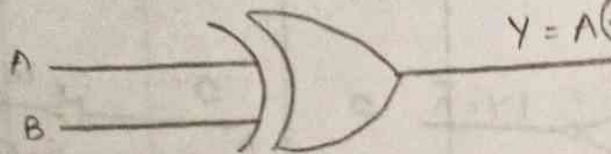

$$Y = A \oplus B = A \cdot \bar{B} + B \cdot \bar{A}$$

(or)

$$Y = \overline{A \odot B}$$


$\downarrow$   
X-NOR

different inputs  
at high side  
input at  
low side

A	B	$\bar{A}$	$\bar{B}$	$Y = A \cdot \bar{B} + B \cdot \bar{A}$
0	0	1	1	$0 + 0 = 0$
0	1	1	0	$0 + 1 = 1$
1	0	0	1	$1 + 0 = 1$
1	1	0	0	$0 + 0 = 0$
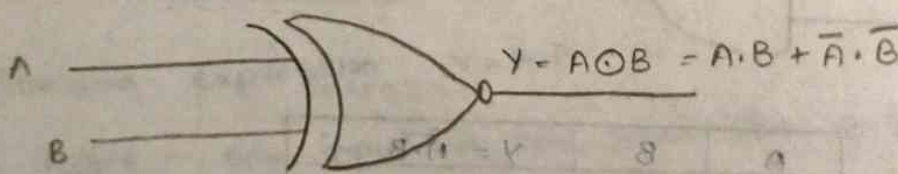
## Exclusive-NOR gate

$$Y = A \odot B \quad (\text{or}) \quad \overline{A \oplus B}$$



$$Y = A \odot B = A \cdot B + \bar{A} \cdot \bar{B}$$

A	B	$\bar{A}$	$\bar{B}$	$A \cdot B$	$\bar{A} \cdot \bar{B}$	$Y = A \cdot B + \bar{A} \cdot \bar{B}$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

Same inputs  
at high  
1 at high  
1 at low

# Realization of Basic gates using universal gates

using NAND gate (NAND gate logic use choti megilónau)

NOT :

NAND Truth table =

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


A not gate Can be made from a NAND gate by connecting all the inputs together and creating a single common input for a two input NAND gate

$B = A$  if  $A = B = X$

$$Y = \overline{A \cdot B}$$



$$= \overline{X \cdot X}$$

$$= \overline{X}$$

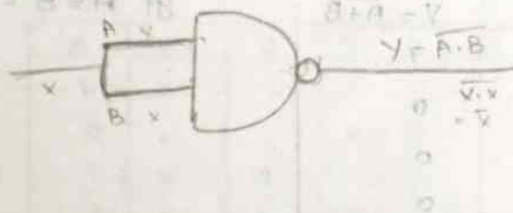

Fix one input at the not gate karne result Vairundhi

## AND function using NAND = AND + NOT

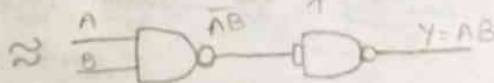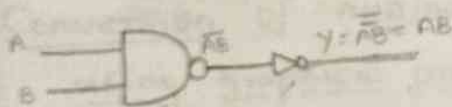

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

$\approx$

A	B	$\overline{A \cdot B}$	$\overline{\overline{A \cdot B}}$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

## OR function :


$$Y = A + B$$

$$= \overline{\overline{A} \cdot \overline{B}}$$

[DeMorgan's Law]

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$
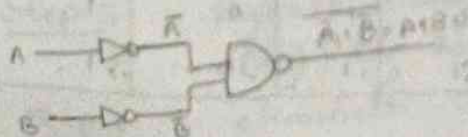
$$\therefore \overline{\overline{A \cdot B}} = A + B$$



# Truth table :-

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1


A	B	$\bar{A}$	$\bar{B}$	$\bar{A} \cdot \bar{B} = \overline{A+B}$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

## Realization of basic gates using NOR

### Not function :-

A	B	$Y = \bar{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

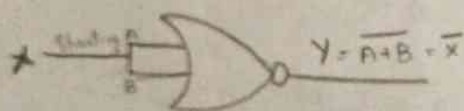gf.  $A=B=X$  then  $Y = \bar{A+B}$   
 $\bar{A+B} = \bar{X+X}$   
 $\bar{X+X} = \bar{X}$




QUALITY of gate Karuika A+B  
 Not with Karuika  
 $\bar{A+B}$

### OR function

NOR  $Y = \bar{A+B}$

$\bar{\bar{A+B}}$   
 $= A+B$

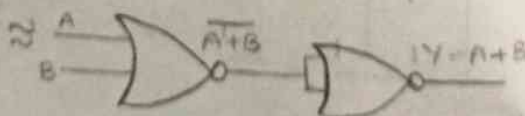

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

A	B	A+B	$\bar{A+B}$	$Y = \bar{\bar{A+B}} = A+B$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1



## AND function

And gate Boolean expression



$$Y = A \cdot B$$

$$= \overline{\overline{A} \cdot \overline{B}}$$

$$Y = \overline{A + B}$$

[from De Morgan's Law]
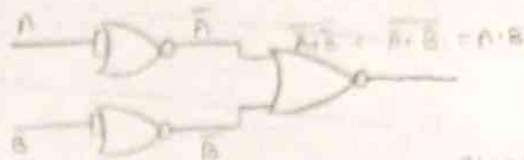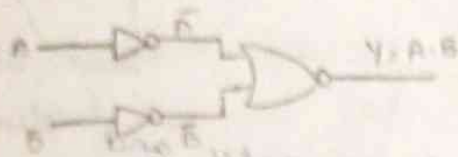
$$\overline{A+B} = \overline{A} \cdot \overline{B}$$



## Truth table

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

A	B	$\overline{A}$	$\overline{B}$	$\overline{A+B}$	$Y = \overline{A+B} = AB$
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

## Conversion of AND/OR/NOT logic to NAND/NOR using graphical procedure:-

Steps:-

Step-1:- Draw and or AND/OR/NOT Logic

Step-2:- If NAND has been chosen add bubbles on the output of each AND gate and bubble on input side of OR gate

Step-3:- If NOR has been chosen add bubbles on output of each OR gate and bubble on input of each AND gate

Step-4:- Add or Subtract an inverter (NOT gate) on each line that received a bubble in Step 2 or Step 3.


Step-5:- Replace bubbled OR by NAND and bubbled AND by NOR

Step-6:- eliminate double inversions

Expression :-


$$\left[ \frac{(A+B)C}{A+B} \right] D$$

Bracket

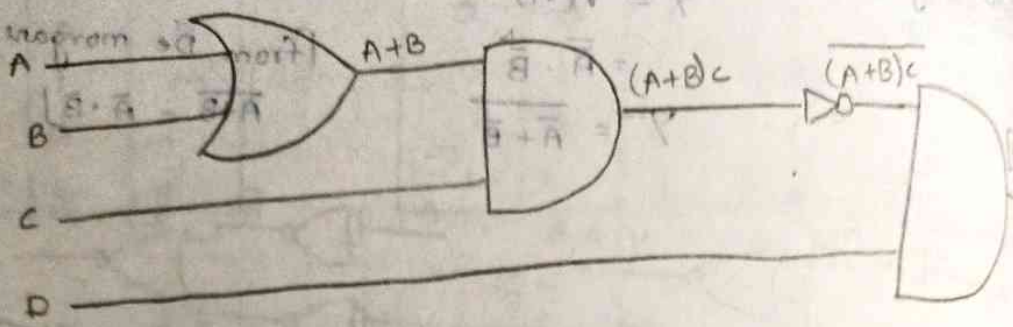


NAND

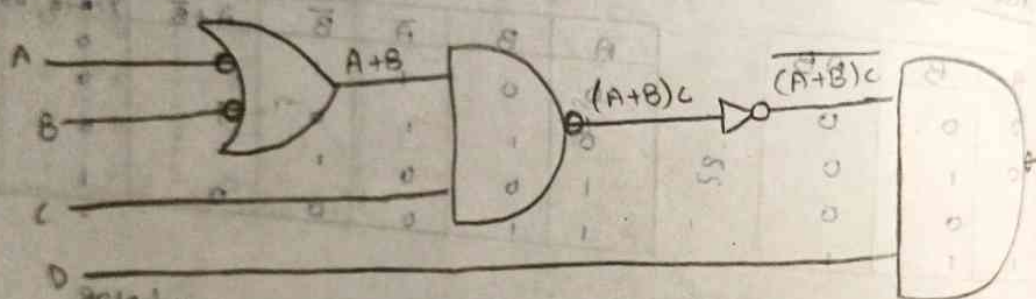
Add bubbles on the inputs of OR gates and output of AND gate



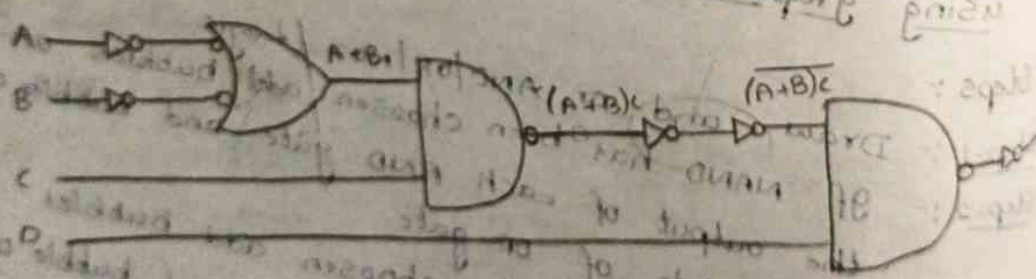Add ~~each~~ inverter on each bubble line that received a bubble




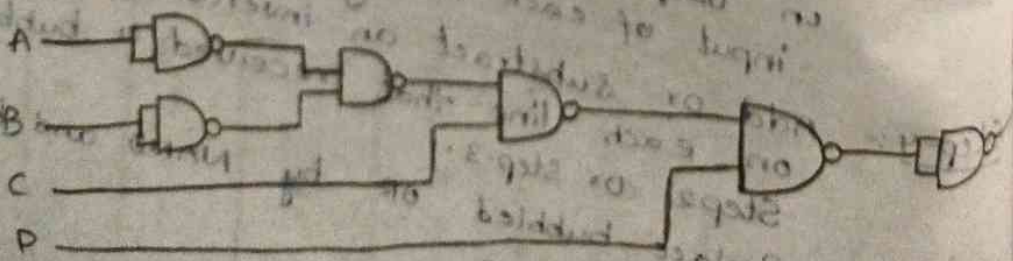Replace double bubble OR by NAND and eliminate double inversions







# NOR

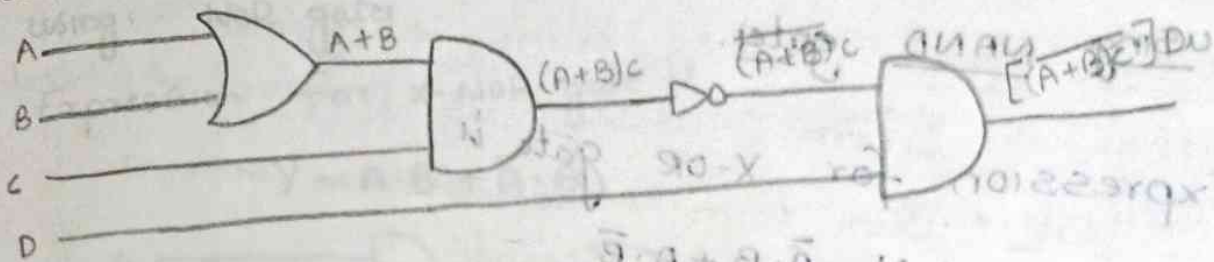

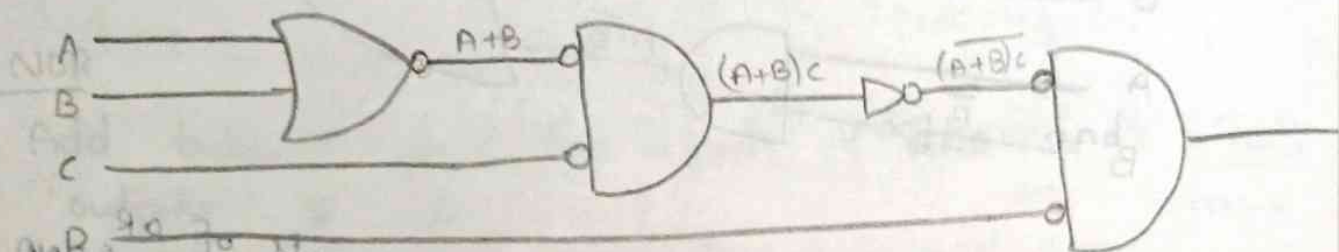
Add bubbles on the inputs of AND gates and output of OR gate



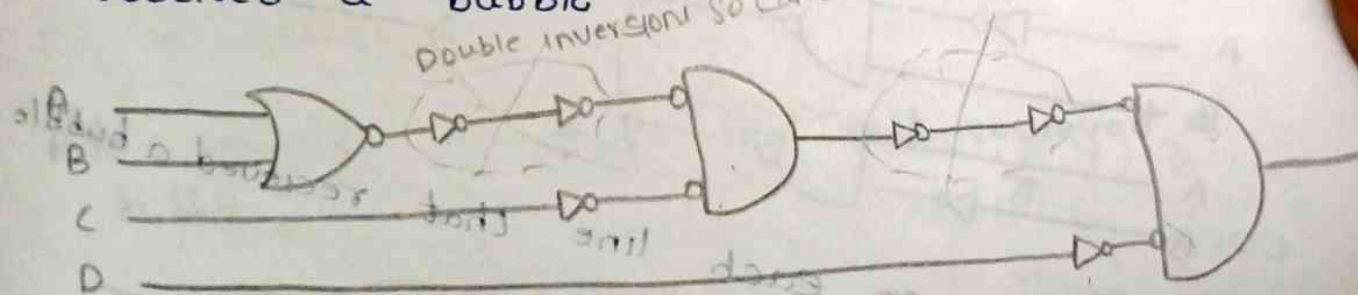Add inverter (not gate) on each line that received a bubble



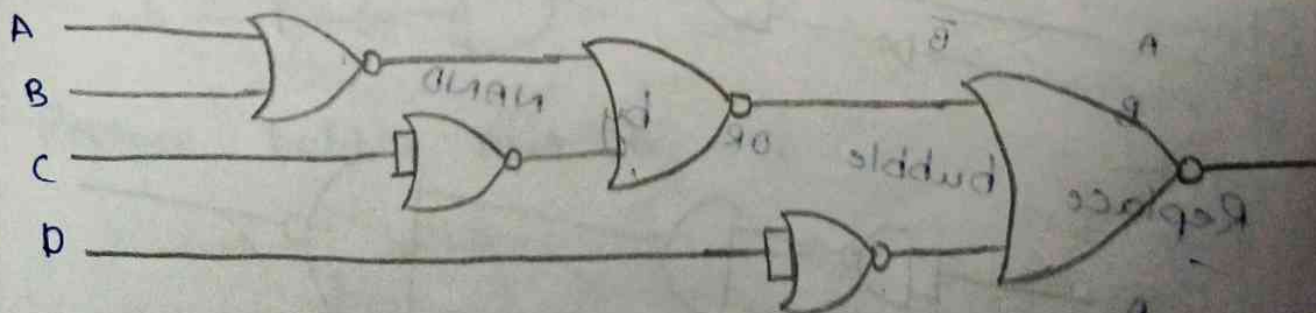
Replace bubble AND by NOR and eliminate double inversions


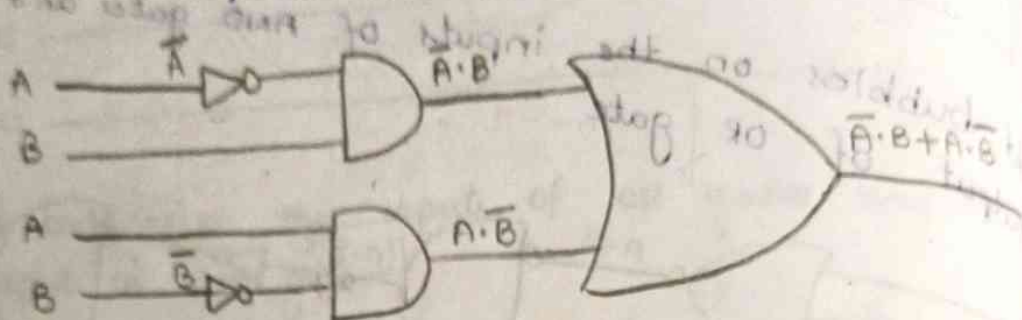
# Implement boolean expression for X-OR gate using NAND gates


Expression for X-OR gate is

$$Y = \bar{A} \cdot B + A \cdot \bar{B}$$




NAND

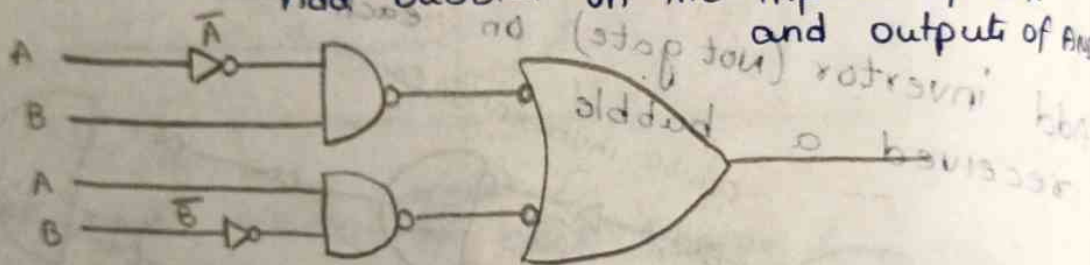
Add bubbler on the inputs of OR and output of AND



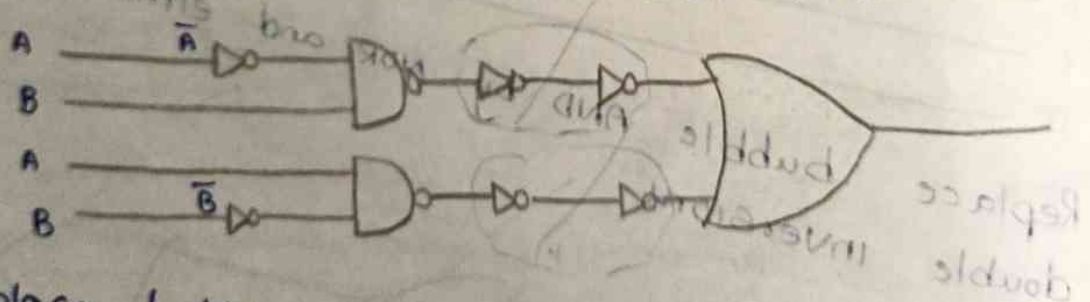Add inverter on each line that recieved a bubble




Replace bubbler OR by NAND

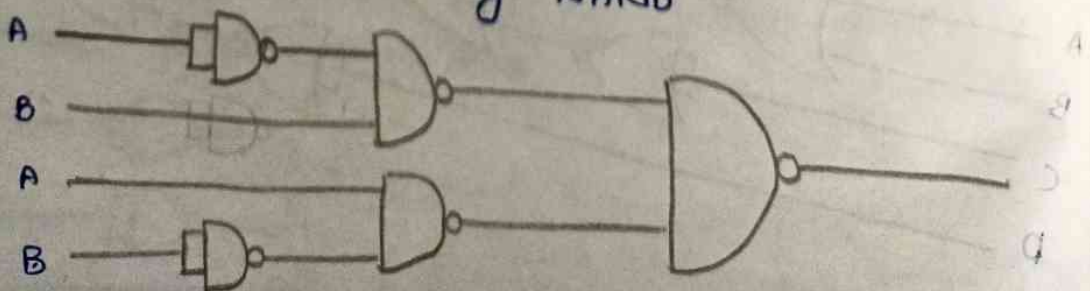

Implement boolean expression for X-NOR gate using NOR gates


Expression for X-NOR gate is
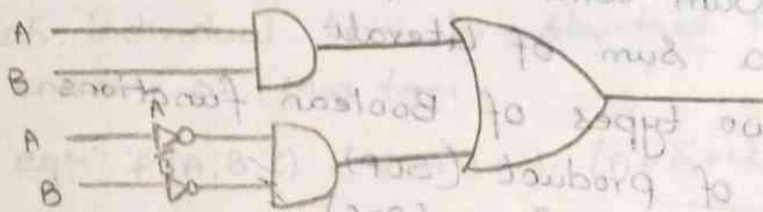
$$Y = A \cdot B + \bar{A} \cdot \bar{B}$$




NOR

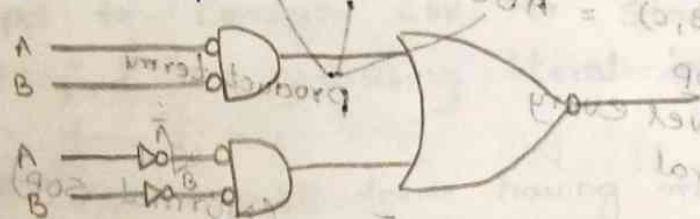
Add bubbler on the inputs of AND and outputs of OR



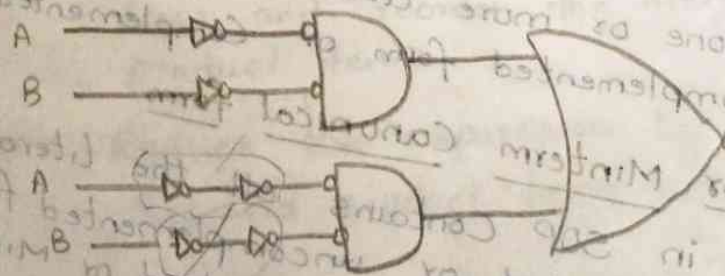Add inverter on each line that recieved a bubble



Replace bubbles AND by NOR

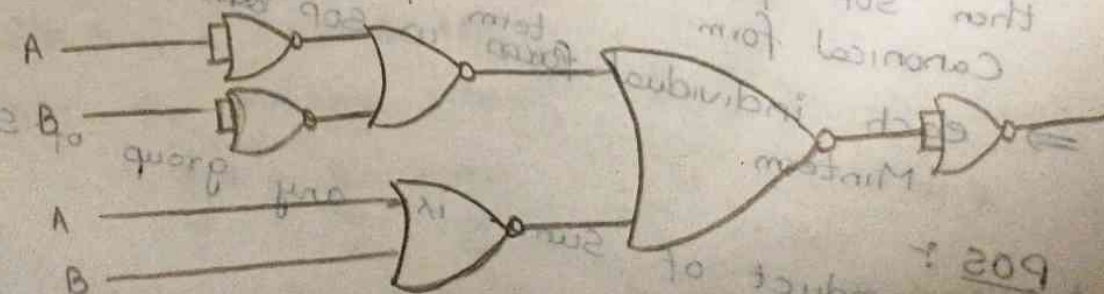



## SOP and POS

Product term:- product term is defined as either a Literal (Variable) or product of Literals.

Sum term:- Sum term is defined as either a Literal or a Sum of Literals.

They are two types of Boolean functions

⇒ Sum of product (SOP)

⇒ product of Sum (POS)

SOP:- A Sum of products is a group of product terms OR together (ORed)

Ex:  $f(A, B, C) = ABC + A\bar{B}C + A\bar{B}\bar{C}$

Standard SOP  
which involves every  
Literal

Diagram: A tree structure showing the expansion of the sum terms. The top level is "Sum terms" with three branches:  $ABC$ ,  $A\bar{B}C$ , and  $A\bar{B}\bar{C}$ . These three branches converge to a single point labeled "product terms".

(ii)  $f(P, Q, R, S) = PQ + \bar{R}S + Q\bar{S}$  (Normal SOP)

each of these SOP expressions consists of 2 or more product terms and each product term consists of one or more Literals appearing in either uncomplemented form or Complemented form

## Standard SOP or Minterm Canonical form

If each term in SOP contains all the Literals either in Complemented or uncomplemented form then SOP form is known as Standard or Minterm Canonical form.

⇒ each individual term in SOP form is called Minterm

## POS:-

⇒ A product of Sum is any group of Sum terms ANDed

$f(A, B, C) = (A+B)(A+\bar{B}+C)$

Diagram: A tree structure showing the expansion of the product terms. The top level is "Sum terms" with two branches:  $(A+B)$  and  $(A+\bar{B}+C)$ . These two branches converge to a single point labeled "product".

## Standard POS term

⇒ If each term in POS contains all the literals either in Complemented form or in uncomplemented form then the POS form is known as Standard POS or Max term. Canonical POS term

⇒ each individual term in Standard POS term form is known as Max term.

$$\text{eg:- } f(A, B, C) = (A+B+C) \cdot (A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})$$

↓  
Sum term or Max term

Converting expressions in Standard SOP or POS forms

1) Steps to Convert SOP to Standard SOP

Step-1:- find the missing literal in each product term if any

Step-2:- "AND" each term having missing literal/literals with term/terms form by "OR'ing the literal and its complement

Step-3:- expand the terms by applying distributive law and reorder the literals in the product terms

Step-4:- Reduce the expression by omitting (Removing) Repeated product terms because  $A+A=A$

Eg-1 Convert the given expression in Standard SOP form

$$i) f(A, B, C) = AB + BC + AC$$

Write the missing literal

$$AB + BC + AC$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$C \quad A \quad B$$

AND the missing literal by OR'ing its complement

$$AB \cdot (C+\bar{C}) + BC \cdot (A+\bar{A}) + AC \cdot (B+\bar{B})$$

$$ABC + AB\bar{C} + BCA + BC\bar{A} + ACB + A\bar{C}B$$

$$ABC + AB\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C$$



omitting the Repeating term

$$ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C$$

Eg-2

$$f(A, B, C) = A + ABC$$

write the missing literals

$$A + ABC$$

$$\downarrow$$
$$BC$$

$$A(B + \bar{B})(C + \bar{C}) + ABC$$

$$A(BC + B\bar{C} + C\bar{B} + \bar{B}\bar{C}) + ABC$$

$$ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC$$

$$ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C}$$

Steps to convert POS form to Standard POS

Step-1 : find the missing literal in each sum term if any

Step-2 : "OR" each sum term having missing literal/literals with term/terms form by AND the literal and its complement

Step-3 : Expand the terms by applying distributive law and reorder the literals in the sum term

Step-4 : Reduce the ~~omitting~~ expression by omitting Repeated sum term by  $A \cdot A = A$

Eg-1 : Convert the given eqn Standard POS

$$f(A, B, C) = (A+B)(B+C)(C+A)$$

write the missing literals

$$(A+B)(B+C)(C+A)$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$= [(A+B) + C \cdot \bar{C}] [(B+C) + A \cdot \bar{A}] [(C+A) + A \cdot \bar{A} B \cdot \bar{B}]$$



from distributive law

$$(A+B+c)(A+B+\bar{c})(B+c+A)(B+c+\bar{A})(\underline{A+B+c})(c+A+\bar{B})$$

$$(A+B+c)(A+B+\bar{c})(\bar{A}+B+c)(A+\bar{B}+c)$$

$$A \cdot (A+B+c)$$

$$\downarrow$$

$$A+B\bar{B}+c\bar{c}$$

$$(A+B+c)(A+B+\bar{c})(A+\bar{B}+c)(A+\bar{B}+\bar{c})$$

K-Map :

⇒ The basis of this method is a graphical chart is known as Karnaugh map (K-Map). It contains boxes called cells.

⇒ Each of the cell represents one of the  $2^n$  possible products that can be formed from  $n$  variables

2 Variables can contain  $2^2 = 4$  cells

3 Variables can contain  $2^3 = 8$  cells

4 Variables can contain  $2^4 = 16$  cells

2 Variable K-Map

$$\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB = A + \bar{A} = 1$$

	$\bar{B}$	$B$
$\bar{A}$	$\bar{A}\bar{B}$ 0	$\bar{A}B$ 1
$A$	$A\bar{B}$ 2	$AB$ 3

3 Variable K-Map

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	$\bar{A}\bar{B}\bar{C}$ 0	$\bar{A}\bar{B}C$ 1	$\bar{A}B\bar{C}$ 3	$\bar{A}BC$ 2
$A$	$A\bar{B}\bar{C}$ 4	$A\bar{B}C$ 5	$ABC$ 7	$AB\bar{C}$ 6

# Variable K-Map

	CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
AB	$\bar{A}\bar{B}\bar{C}\bar{D}$ 0000 0	$\bar{A}\bar{B}\bar{C}D$ 0001 1	$\bar{A}\bar{B}C\bar{D}$ 0011 3	$\bar{A}\bar{B}CD$ 0010 2	
$\bar{A}B$	$\bar{A}B\bar{C}\bar{D}$ 0100 4	$\bar{A}B\bar{C}D$ 0101 5	$\bar{A}BC\bar{D}$ 0111 7	$\bar{A}BCD$ 0110 6	
AB	$AB\bar{C}\bar{D}$ 1100 12	$AB\bar{C}D$ 1101 13	$ABC\bar{D}$ 1111 15	$ABCD$ 1110 14	
$\bar{A}\bar{B}$	$A\bar{B}\bar{C}\bar{D}$ 1000 8	$A\bar{B}\bar{C}D$ 1001 9	$A\bar{B}C\bar{D}$ 1011 11	$A\bar{B}CD$ 1010 10	

2 cells grouping

AB	CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	1	3	2
$\bar{A}B$	1	4	5	7	6
AB	12	13	15	14	
$\bar{A}\bar{B}$	1	9	11	10	

$$= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{C} + A\bar{B}\bar{D}$$

$$= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{D}$$

$$= \bar{B}\bar{C} (A + \bar{A}) + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{D}$$

$$= \bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{D}$$



1) Minimise the expression  $Y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$   
using K-map method

BC	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	1	1	1	0
A	1	1	0	0

$$Y = \bar{B} + \bar{A}C$$

2) Simplify the Boolean function  $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	0	1
$\bar{A}B$	1	1	0	1
$AB$	1	1	1	1
$A\bar{B}$	1	1	0	0

$$Y = \bar{C} + AB\bar{D} + C\bar{D}A$$

$$= AB\bar{D} + \bar{A}\bar{C}\bar{D} + \bar{C}$$

3)  $f(A, B, C, D) = \sum m(0, 1, 2, 3, 11, 12, 14, 15)$

CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	0	0	0	0
$AB$	1	0	1	1
$A\bar{B}$	0	0	1	0

$$Y = \bar{A}\bar{B} + ACD + AB\bar{D}$$



POS  
 Tm (0, 2, 3, 8, 9, 12, 13, 15)

AB \ CD	C+D	C+D̄	C̄+D̄	C̄+D
A+B	0	1	3	2
A+B̄	4	5	7	6
Ā+B̄	0	0	0	14
Ā+B	0	0	11	10

quite opp to SOP

Bar Vunte SOP lo  
 ikkada pos lo  
 bar Radhu  
 • ki badhulu

$$Y = (A+B+D) \cdot (\bar{A}+C) \cdot (\bar{A}+\bar{B}+\bar{D}) + (A+B+\bar{C})$$