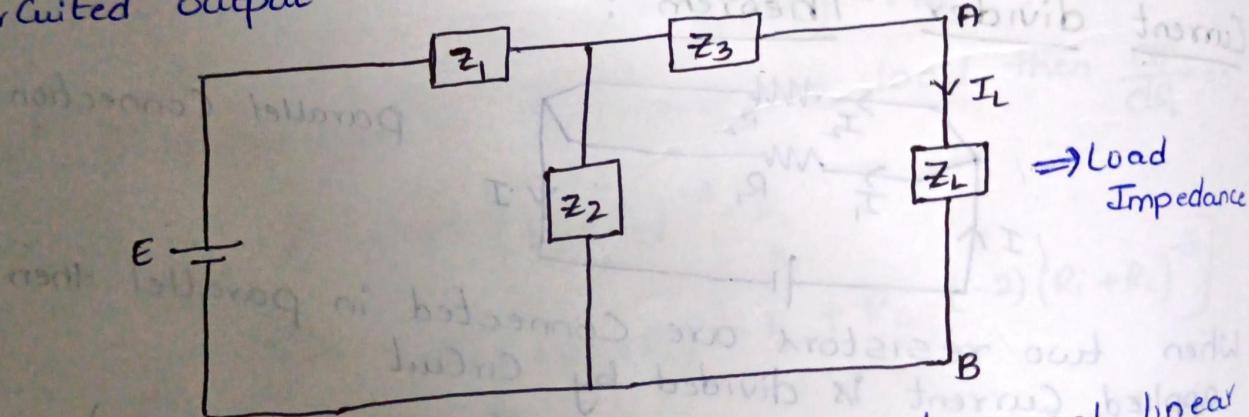


Norton's Theorem :- parallel

Any Linear Active Network Containing Linear Impedance and Voltage Sources Can be replaced by Norton's equivalent circuit.

- ⇒ the Norton's equivalent circuit consists Norton's Constant Current Source (I_n) in parallel with Norton's Impedance
- ⇒ Norton's Impedance is the Resultant Impedance between output terminals (Apply cheze param ga Vachedi)
- When all Voltage Sources Can be replaced by their Internal Impedances if any
- ⇒ Norton's Current is Current passing through the Short Circuited output.




The above figure shows that the two terminal linear network it consists a voltage source "E" Linear Impedances z_1, z_2, z_3 & Z_L

- ⇒ The Z_L is connected b/w A & B terminals we need to calculate the current passing through the Z_L using Norton's theorem has follows.


Norton's equivalent Circuit

I_n = Norton's Current

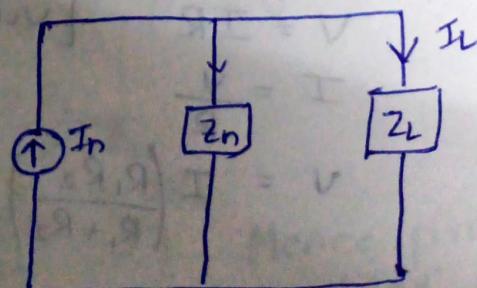

According to Norton's theorem the Norton's equivalent Circuit consists the Norton's Constant Current Source (I_N) in parallel with Norton's Impedance (Z_N)

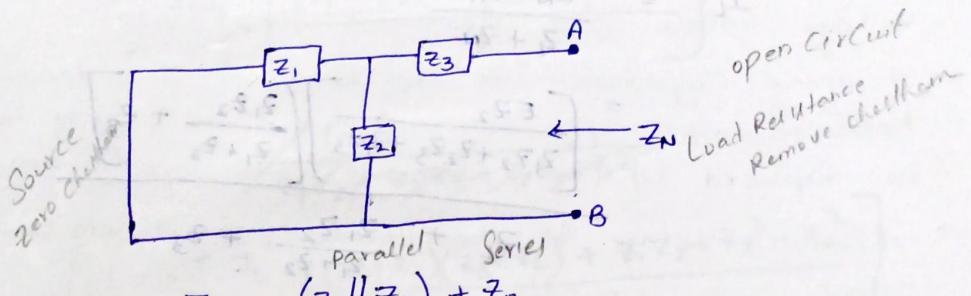
$$I_L = \frac{I_N Z_N}{Z_L + Z_N} \quad \rightarrow ① \quad \text{[As per Current divider theorem]}$$



$$Z_N = (Z_1 \parallel Z_2) + Z_3$$

$$Z_N = \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_3 \quad \rightarrow ②$$

As per Norton's Current

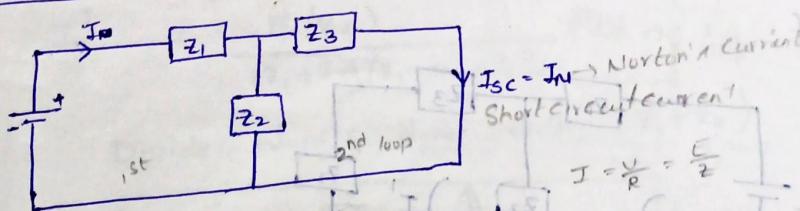

Z = Total Impedance

$$= (Z_2 \parallel Z_3) + Z_1$$

$$= \frac{Z_2 Z_3}{Z_2 + Z_3} + Z_1$$

$$Z = \frac{Z_2 Z_3 + Z_1 Z_2 + Z_1 Z_3}{Z_2 + Z_3}$$

$$\text{Total Current } I = \frac{E_{ab}}{Z}$$

$$I = \frac{E(Z_2 + Z_3)}{Z_2 Z_3 + Z_1 Z_2 + Z_1 Z_3}$$

Norton's Current

$$I_N = \frac{I Z_2}{Z_2 + Z_3}$$

across $Z_2 \& Z_3$

$$(2^{\text{nd}} \text{ loop only}) = \frac{E(Z_2 + Z_3)}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3} \left(\frac{Z_2}{Z_2 + Z_3} \right)$$

Short circuit

$$I_N = \frac{EZ_2}{Z_1Z_2 + Z_2Z_3 + Z_1Z_3}$$

→ ③

Sub ② + ③ in eq - ①


$$I_L = \frac{I_N \cdot Z_N}{Z_L + Z_N}$$

$$= \left[\frac{EZ_2}{Z_1Z_2 + Z_2Z_3 + Z_1Z_3} \right] \left[\frac{Z_1Z_2}{Z_1 + Z_2} + Z_3 \right]$$

$$= Z_L + \frac{Z_1Z_2}{Z_1 + Z_2} + Z_3$$

$$I_L = \frac{EZ_2 / Z_1 + Z_2}{Z_L + Z_3 + \frac{Z_1Z_2}{Z_1 + Z_2}}$$

Proof: As per KVL

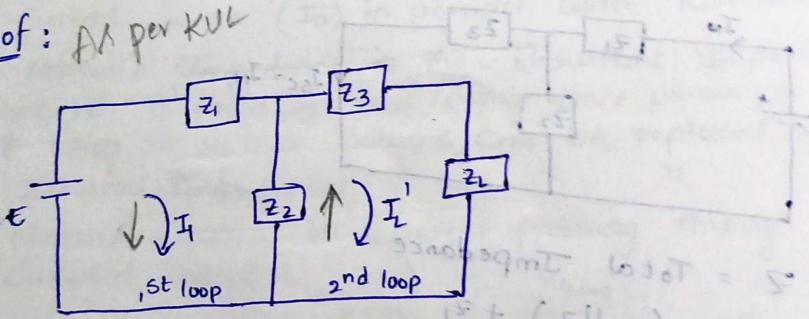

Apply KVL to 1st Loop

$$E = I_1 Z_1 + Z_2 (I_1 - I_L')$$

$$= I_1 Z_1 + I_1 Z_2 - I_L' Z_2$$

$$= I_1 (Z_1 + Z_2) - I_L' Z_2 \quad \rightarrow ①$$

Apply KVL to 2nd Loop

$$0 = I_L' Z_3 + Z_L I_L' + Z_2 (I_L' - I_1)$$

$$= I_L' Z_3 + I_L' Z_L + I_L' Z_2 - I_1 Z_2$$

$$= I_L' (Z_2 + Z_3 + Z_L) - I_1 Z_2$$

$$I_1 = \frac{I_L' (Z_2 + Z_3 + Z_L)}{Z_2} \quad \rightarrow ③$$

Sub I_1 value in eq (1)

$$E = I_L' \frac{(z_2 + z_3 + z_L)(z_1 + z_2)}{z_2} - I_L' z_2$$

$$= I_L' \left[\frac{(z_1 + z_2)(z_2 + z_3 + z_L)}{z_2} - z_2 \right]$$

$$= I_L' \left[\frac{(z_1 + z_2)(z_2 + z_3 + z_L) - z_2^2}{z_2} \right]$$
~~$$I_L' = \frac{E(z_2)}{z_1 z_2 + z_2 z_3 + z_1 z_3 + z_1 z_L}$$~~

$$= I_L' \left[\frac{(z_1 + z_2)(z_3 + z_L) + z_1 z_2 + z_2^2 - z_2^2}{z_2} \right]$$

$$E = I_L' \left[\frac{(z_1 + z_2)(z_3 + z_L) + z_1 z_2}{z_2} \right]$$

$$I_L' = \frac{E(z_2)}{(z_1 + z_2)(z_3 + z_L) + z_1 z_2}$$

Divide Num & deno with $(z_1 + z_2)$


$$\boxed{I_L' = \frac{\frac{E z_2}{z_1 + z_2}}{z_L + z_3 + \frac{z_1 z_2}{z_1 + z_2}}}$$

$$\therefore I_L = I_L'$$

Hence proved

Maximum power transform theorem:

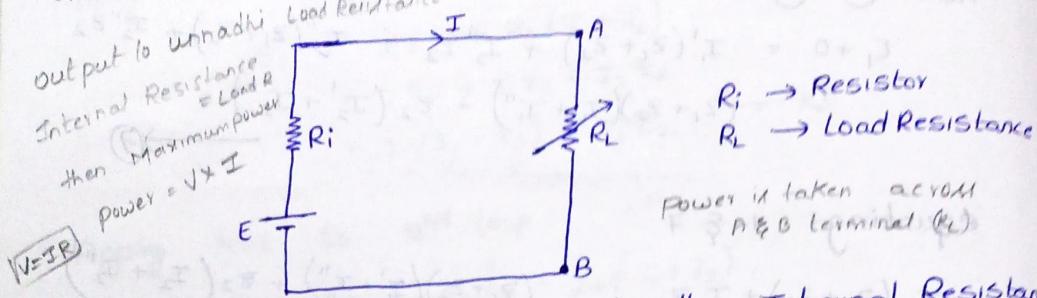In an Active Network the Maximum power delivered to load when the Internal Resistance of Source or Network is equals to Load Resistance



In this active Network R_i is the Internal Resistance of Source and R_L is the Load Resistance

$$\text{Total Resistance } R = R_i + R_L$$

$$\text{Current passing through the circuit } I = \frac{E}{R_i + R_L}$$

power delivered to the load

$$P = V \times I \\ = IR \times I \\ \therefore V = IR$$

$$= I^2 R_L \quad [R = R_L \text{ because power is taken across A & B}]$$

$$P = \left[\frac{E}{R_i + R_L} \right]^2 \cdot R_L$$

$$P = E^2 (R_i + R_L)^{-2} \cdot R_L$$

When maximum power delivered to load then $\frac{dP}{dR_L} = 0$

$$P = E^2 (R_i + R_L)^{-2} \cdot R_L$$

$$\frac{dP}{dR_L} = E^2 \left[(R_i + R_L)^{-2} \cdot 1 + R_L (-2)(R_i + R_L)^{-3} \right]$$

$$= E^2 \left[(R_i + R_L)^{-2} - 2(R_i + R_L)^{-3} \cdot R_L \right] = 0$$

$$E^2 \neq 0 \quad ; \quad R_i + R_L \neq 0 \quad [\text{Applied source so } \neq 0]$$

$$E^2 \left[(R_i + R_L)^{-2} \left(1 - 2(R_i + R_L)^{-1} \cdot R_L \right) \right] = 0$$

$$1 - 2(R_i + R_L)^{-1} \cdot R_L = 0$$

$$1 = \frac{2 R_L}{R_i + R_L}$$


$$R_i + R_L = 2 R_L$$

$$R_i = R_L$$

Hence proved
Max power is delivered

Reciprocity Theorem :-

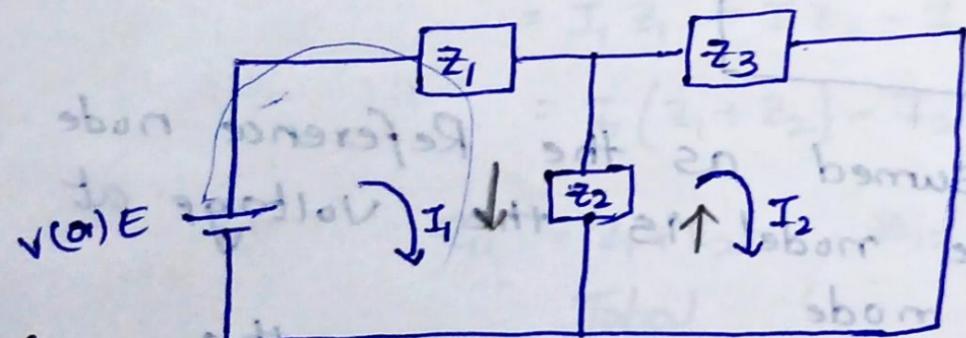Statement: Any Active Linear network Contains Linear Impedances, If EMF is Applied in the first Loop then the Current passing through the Second loop is equals to Current flowing through the first loop when the Same Source Acting in the Second Loop



Linear Active - Voltage

Proof :-

Apply KVL to 1st Loop $I_1' = I_2$

$$E = I_1 z_1 + z_2(I_1 - I_2)$$

$$= I_1 z_1 + I_1 z_2 - I_2 z_2$$

$$= I_1(z_1 + z_2) - I_2 z_2 \longrightarrow ①$$

Apply KVL to 2nd Loop

$$0 = I_2 z_3 + z_2(I_2 - I_1)$$

$$= I_2 z_3 + I_2 z_2 - I_1 z_2$$

$$= I_2(z_2 + z_3) - I_1 z_2 \longrightarrow ②$$

$$I_2(z_2 + z_3) = I_1 z_2$$

$$I_1 = \frac{I_2(z_2 + z_3)}{z_2} \longrightarrow ③$$

Sub ③ in ①

$$E = I_1(z_1 + z_2) - I_2 z_2$$


$$= \frac{I_2(z_2 + z_3)(z_1 + z_2)}{z_2} - I_2 z_2$$

$$= \frac{(I_2 z_2 + I_2 z_3)(z_1 + z_2) - I_2 z_2^2}{z_2}$$

$$= \frac{I_2 z_2 z_1 + I_2 z_2^2 + I_2 z_1 z_3 + I_2 z_2 z_3 - I_2 z_2^2}{z_2}$$

$$= \frac{I_2(z_1 z_2 + z_2 z_3 + z_1 z_3)}{z_2}$$
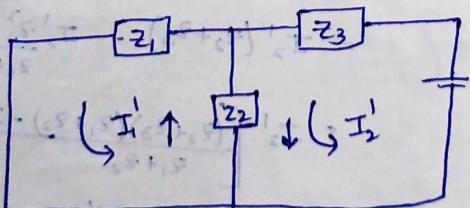
$$I_2 = \frac{E z_2}{z_1 z_2 + z_2 z_3 + z_1 z_3}$$



Currents in opp direction

Apply KVL to 1st loop

$$0 = I_1' z_1 + (I_1' - I_2') z_2$$

$$= I_1' z_1 + I_1' z_2 - I_2' z_2$$

$$= I_1'(z_1 + z_2) - I_2' z_2$$

$$I_2' = \frac{I_1'(z_1 + z_2)}{z_2} \longrightarrow ④$$

$$E = I_2' z_3 + z_2(I_2' - I_1')$$

$$= I_2' z_3 + I_2' z_2 - I_1' z_2$$

$$E = I_2' (z_2 + z_3) - I_1' z_2 \rightarrow ⑥$$

Sub eq (4) in ⑤

~~$$E = I_2' (z_2 + z_3) - I_1' z_2$$~~

$$= \frac{I_1' (z_1 + z_2)(z_2 + z_3)}{z_2} - I_1' z_2$$

$$= \frac{(I_1' z_1 + I_1' z_2)(z_2 + z_3)}{z_2} - I_1' z_2^2$$

$$\leftarrow = \frac{I_1' z_1 z_2 + I_1' z_1 z_3 + I_1' z_2^2 + I_1' z_2 z_3 - I_1' z_2^2}{z_2}$$

$$= \frac{I_1' (z_1 z_2 + z_2 z_3 + z_1 z_3)}{z_2}$$

$$\boxed{I' = \frac{E z_2}{z_1 z_2 + z_2 z_3 + z_1 z_3}}$$


$$\therefore \boxed{I' = I_2}$$

Hence proved

Millman's Theorem :

Millman's theorem states that a network containing no of voltage sources having series impedances are connected in parallel then such a network can be reduced to a single network containing one voltage source and impedance.

Consider a network shown in figure

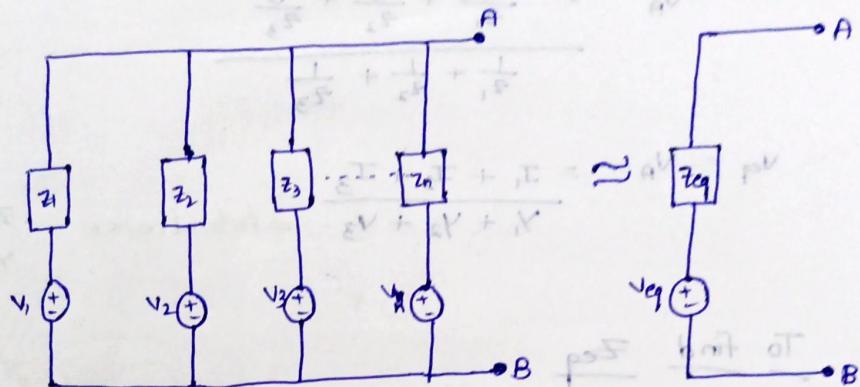

Where

$$V_{eq} = \frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3} + \dots + \frac{V_n}{Z_n}$$

$\sum \frac{1}{Z_i}$


$$= I_1 + I_2 + I_3 + \dots + I_n$$

$$Z = \frac{V}{I}$$

$$Y = \text{Admittance} = \frac{1}{Z} = \frac{I}{V}$$

$$V_{eq} = \frac{\sum_{i=1}^n I_i}{\sum_{i=1}^n Y}, \quad Z_{eq} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$

Proof

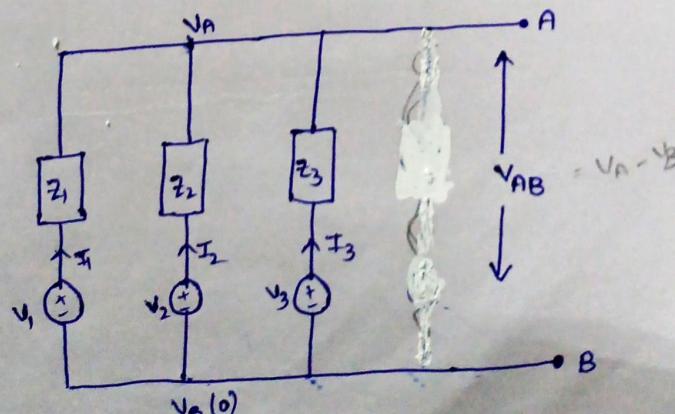

Ground (Reference Node) = 0

Apply KCL at nodes

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_A - V_1}{Z_1} + \frac{V_A - V_2}{Z_2} + \frac{V_A - V_3}{Z_3} = 0$$

$$V_A \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) - \left(\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3} \right) = 0$$


$$\frac{V_A}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

$$V_{eq} = V_A = \frac{I_1 + I_2 + I_3}{Y_1 + Y_2 + Y_3}$$

\Rightarrow Admittance

$$Y = \frac{I}{V}$$

To find Z_{eq}

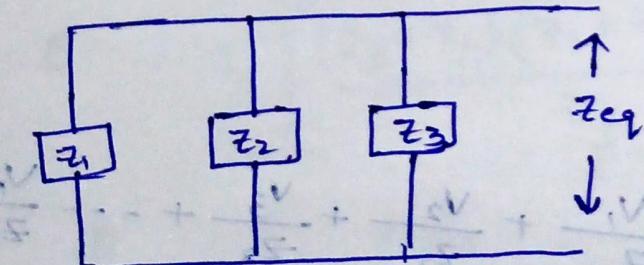

They are in parallel

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$Z = \frac{Z_1 Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

$$Z = \frac{Z_1 Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$$

passive Networks

Circuit :- A circuit is a closed path through which an electric current either flows or intend to flow

↓
try

Electrical Network : The combination of various electronic components connected in any manner is called as electrical network

↓
closed/open

passive Network : If a network contains circuit elements (components) without any source that is voltage (or) current source

Active Network : If a network contains circuit elements with energy source is called as Active Network.

↓
Voltage (or) Current

⇒ They are two types of Active Networks


- 1. Linear Active Network
- 2. Non linear Active Network

Linear Active Network : A Network is said to be linear when currents in all branches linearly proportional to driving voltage. (apply ohm's law)

Non-Linear Network : A Network is said to be Non-linear when currents in all branches Non-linearly proportional to driving voltage.

Integrated Circuit : Semi Conductor circuit with silicon chip

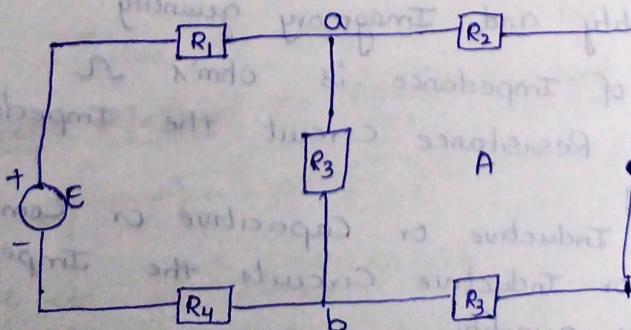Node :- The junction points where the elements in a network meet such as the points a and b




Branch :- An element joining two nodes such as a to b is called a Branch.

Loop :- Any closed path in a network such as abc... is called a loop.

Mesh :- The Space that the loop encloses is called a Mesh.

Kirchoff's Current Law :- The Algebraic sum of currents meeting at a point (Node) is zero.

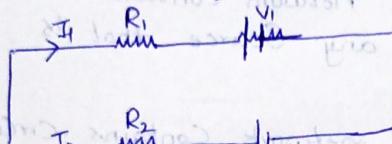Kirchoff's Voltage Law :- The Algebraic sum of voltage drop is equal to the EMF's of the Resistors.



$$V_1 + V_2 = I_1 R_1 + I_2 R_2$$

$$V = IR$$

Impedance (z) :- $z = \frac{V}{I}$ If only Resistor in Circuit the
 z is Real; if there exist Capacitor, Inductor etc then z has Complex Constants then

Admittance (y) :- $y = \frac{I}{V}$

Series Combination :- $R = R_1 + R_2 + R_3$

Current flow same, Voltage divider

parallel Combination :- $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Voltage flow same, Current divider (different)

Impedance :- Ratio of Voltage and Current

$$z = \frac{V}{I}$$

⇒ The Impedance is the Complex quantity and it consists of Real quantity and Imaginary quantity

units of Impedance is "ohm's" Ω

⇒ for a pure Resistance circuit the Impedance is Real quantity


⇒ for a pure Inductive or Capacitive or Combination of Capacitive or Inductive Circuits the Impedance is Imaginary quantity

⇒ When the Circuit Containing Resistive and Inductive the Impedance is Complex quantity

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$

Branch Current method :-

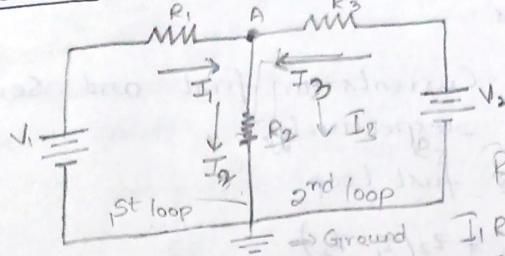

Junct \rightarrow cur
Loop \rightarrow Vol

At node point A

$$I_1 + I_3 - I_2 = 0 \rightarrow \textcircled{1}$$

$$R_2 (I_2 + I_3)$$

$$I_1 R_1$$

At node \rightarrow Current Law

At Loop \rightarrow Voltage Law

$$\text{1st loop } V_1 = I_1 R_1 + I_2 R_2 \quad \text{if } V_1 \text{ is not there then } I_1 R_1 + I_2 R_2 = 0$$

$$\text{2nd loop } V_2 = I_3 R_3 + I_2 R_2$$

\Rightarrow The first and most straight forward network analysis technique is called the branch current method.

\Rightarrow In this method we assume directions of currents in a network then write equations describing their relationship to each other through Kirchoff's and Ohm's Law. ($V = IR$)

\Rightarrow Once we have one equation for every unknown current we can solve the simultaneous equations and determine all currents and all voltage drops in the network.

At node point A, Apply KCL

$$I_1 + I_3 - I_2 = 0 \rightarrow \textcircled{1}$$

Apply KVL to 1st loop


$$V_1 = I_1 R_1 + I_2 R_2 \rightarrow \textcircled{2}$$

Apply KVL to 2nd loop

$$V_2 = I_3 R_3 + I_2 R_2 \rightarrow \textcircled{3}$$

Solve the above 3 eqn's by using elimination method

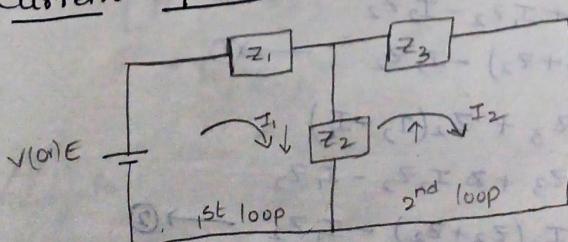Loop Current Method or Mesh Current Method :



OPPOSITE in direction
At 1st loop (1st - 2nd)

\Rightarrow In loop current method the unknown currents are assumed to be flowing around the closed loop in

the network and write the voltage egn in a closed loop as follows

Let us assume the currents in first and second loops are I_1 & I_2 respectively

Apply KVL to the first Loop

$$\begin{aligned} E &= I_1 z_1 + z_2(I_1 - I_2) \\ &= I_1 z_1 + I_1 z_2 - I_2 z_2 \\ &= I_1(z_1 + z_2) - I_2 z_2 \longrightarrow \textcircled{1} \end{aligned}$$

$$\begin{aligned} z_{11} &= z_1 + z_2 & z_{12} &= z_2 \\ \text{Total} & \\ \text{Impedance} & \\ \text{in first loop} & \end{aligned} \quad \begin{aligned} &= \text{Common Impedance} \\ &\text{b/w first \& second} \\ &\text{loop} \end{aligned}$$

Apply KVL to the Second Loop

$$0 = I_2 z_3 + z_2(I_2 - I_1)$$

$$= I_2 z_3 + I_2 z_2 - I_1 z_2$$


$$0 = I_2(z_2 + z_3) - I_1 z_2 \longrightarrow \textcircled{2}$$

$$\textcircled{2} = -I_1 z_2 + I_2(z_2 + z_3) \longrightarrow \textcircled{2}$$

$$z_{21} = z_2 \quad z_{22} = z_2 + z_3$$

$$\begin{aligned} \text{Common Impedance} & \\ \text{b/w 1st \& 2nd loop} & \end{aligned} \quad \begin{aligned} &= \text{Total Impedance} \\ &\text{in the second} \\ &\text{loop} \end{aligned}$$
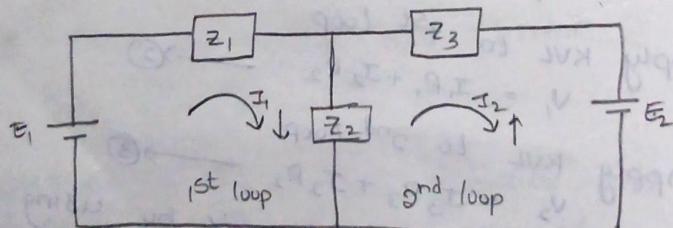
$$\begin{bmatrix} E \\ 0 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$




$$\begin{aligned} E_1 &= I_1 z_1 + z_2(I_1 - I_2) \\ &= I_1 z_1 + I_1 z_2 - I_2 z_2 \\ &= I_1(z_1 + z_2) - I_2 z_2 \longrightarrow \textcircled{1} \end{aligned}$$

$$\begin{aligned} E_2 &= I_2 z_3 + z_2(I_2 - I_1) \\ &= I_2 z_3 + I_2 z_2 - I_1 z_2 \\ &= I_2(z_3 + z_2) - I_1 z_2 \longrightarrow \textcircled{2} \end{aligned}$$


Nodal Analysis :-

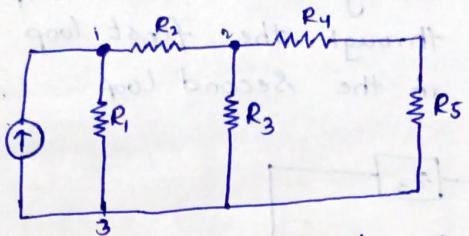The Node Voltage is the voltage of a given node with respect to one particular node called the Reference node which are assume at zero potential.



- ⇒ The node 3 is assumed as the Reference node.
- ⇒ The Voltage at the node is the voltage at that node w.r.t the node.
- ⇒ Similarly the voltage as the node 2 is the voltage at that node w.r.t the node-3.

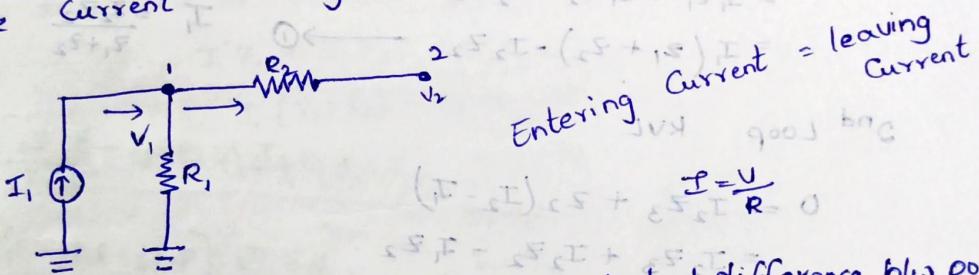
Apply Kirchoff's Current Law as the current leaving the current entering is equal to the current leaving



$$I_1 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} \Rightarrow \text{potential difference b/w points}$$

Node 1 Consider Chettunam
Kenka $V_1 - V_2$ at node 1 & 2

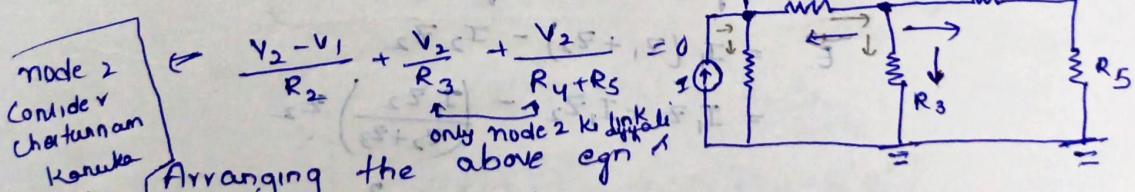Here V_1 and V_2 are the voltages at node 1 & 2. At node 2, the current entering is equal to the current leaving



Arranging the above eqn

$$V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - V_2 \left[\frac{1}{R_2} \right] = I_1$$

$$-V_1 \left[\frac{1}{R_1} \right] + V_2 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4 + R_5} \right] = 0$$

R2 are
Resistor
two
nodes points
ki madyalu
vundhi