

### Unit-3: Voltage Multipliers

- A electronic circuit consisting of diodes and capacitors and converts an AC electric signal from a lower voltage to a higher DC voltage value is referred as a Voltage Multiplier.

⇒ These circuits increases the input voltage of level ' $V_m$ ' to an output of ' $n$ ' times of ' $V_m$ '.

$$\Rightarrow \boxed{V_o = n V_m}$$

if  $n=2 \Rightarrow$  it's referred as voltage Doubler.

if  $n=3 \Rightarrow$  it's called as voltage Tripler.

if  $n=4 \Rightarrow$  it's called as voltage Quadrapler.

⇒ Here in the Voltage multipliers, it performs both rectification and multiplication of voltage.


⇒ Rectification is done by rectifier = Diode  
multiplication is done by capacitors.

#### Voltage Doubler-

The electronic circuit which multiplies the input voltage by '2' times (i.e) doubles the input voltage is called a Voltage Doubler.

They are two types - Halfwave Voltage Doubler  
- Fullwave voltage Doubler

#### Half-wave Voltage Doubler -

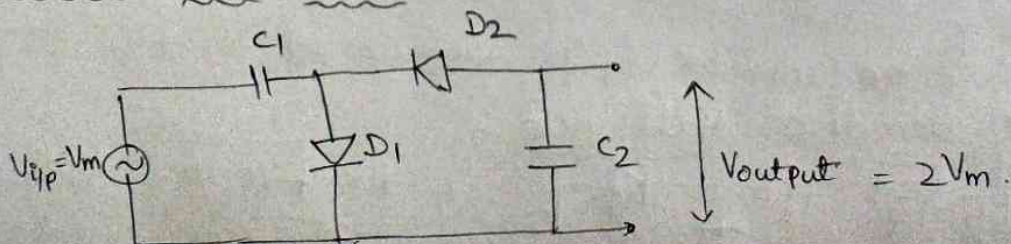



- As the name indicates, a voltage doubler is a voltage which doubles the input voltage.

- It consists of two capacitors and two diodes.

- Thus it's a two-stage voltage multiplier.

The working of above circuit is as follows.

→ for +ve half cycle of the input

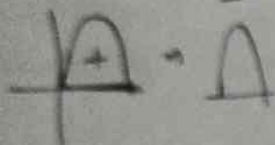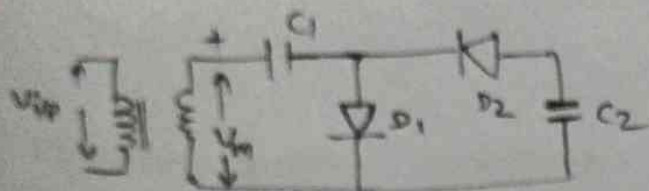


the  $D_1$  diode is forward biased  
 $D_2$  diode is reverse biased

$\Rightarrow D_1 \rightarrow \text{ON} \Rightarrow \text{SC}$  (short circuited)

$D_2 \rightarrow \text{OFF} \Rightarrow \text{OC}$  (open circuited)

we redraw the circuit

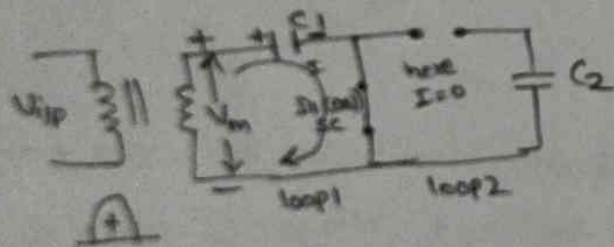

then applying the KVL '1'


$$\rightarrow +V_m - V_{C1} = 0$$

$$\therefore \boxed{V_{C1} = +V_m}$$

$V_m \Rightarrow$  peak or maximum  
 i/p voltage value.

$\Rightarrow$  the capacitor  $C_1$  is fully charged to  $+V_m$  volts.

\* for Negative Half cycle -

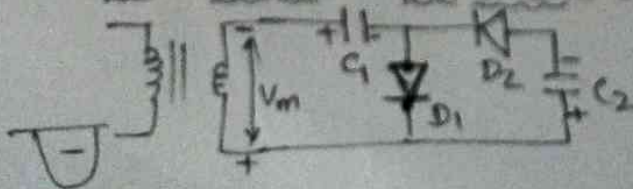


for +ve Half cycle

$D_1 \rightarrow \text{OFF (RB)} \rightarrow \text{OC}$

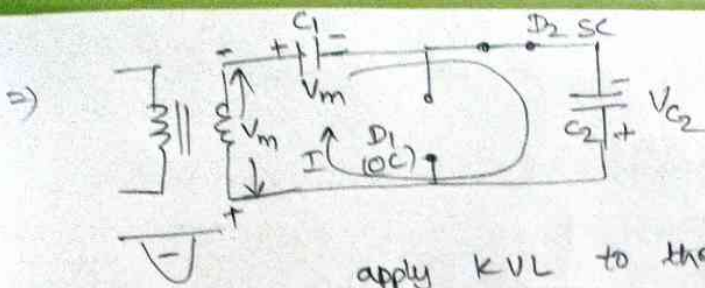$D_2 \rightarrow \text{ON (FB)} \rightarrow \text{SC}$





apply KVL to the above loop

$$\text{we get } -V_m - V_m + V_{C_2} = 0$$

$$\Rightarrow -2V_m + V_{C_2} = 0$$

$$\therefore \boxed{V_{C_2} = 2V_m}$$


∴ the o/p voltage ⇒ capacitance voltage =  $2V_m$

→ thus the output voltage is double or 2 times that of the input voltage ( $V_m$ ).
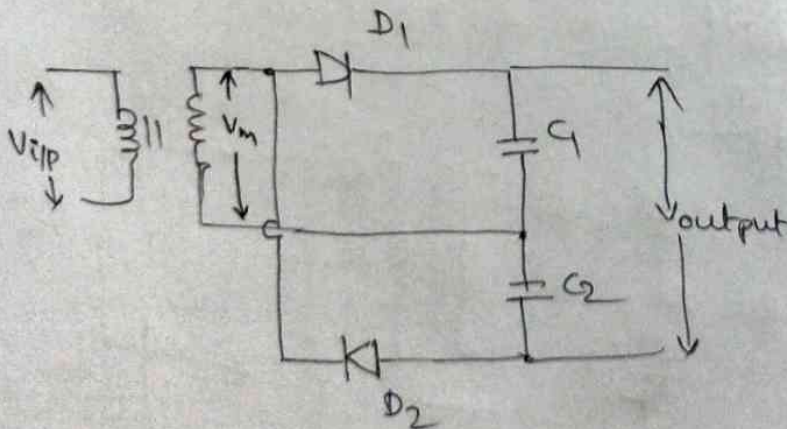
### ⇒ Full-wave Voltage Doubler

A full wave voltage doubler simply resembles a full wave rectifier (center-tapped).

It uses a center-tapped transformer for the input.





the above circuit is a fullwave voltage doubler

it consists of 2 capacitors, 2 diodes

working -

→ For +ve half cycle.

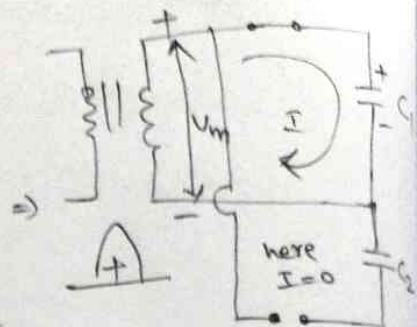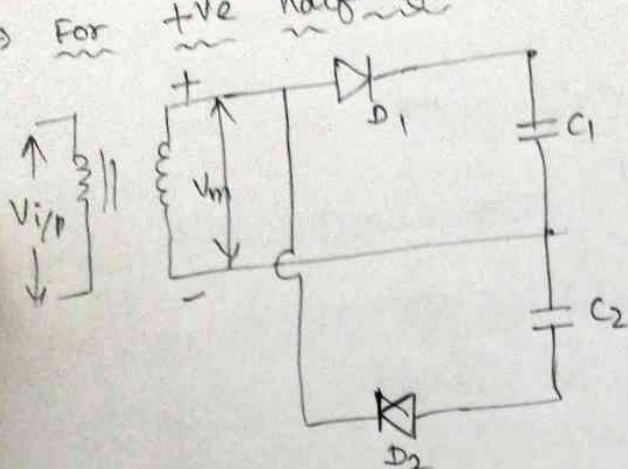

the  $D_1 \rightarrow F.B \rightarrow ON \rightarrow SC$

$D_2 \Rightarrow R.B \rightarrow OFF \rightarrow OC$



$\therefore$  the KVL for the above loop is

$$+V_m - V_{C1} = 0$$

$$\therefore V_{C1} = V_m$$

$\Rightarrow$  the capacitor  $\rightarrow C_1$  will be charged to  $V_m$ .

→ for negative half cycle of the input -

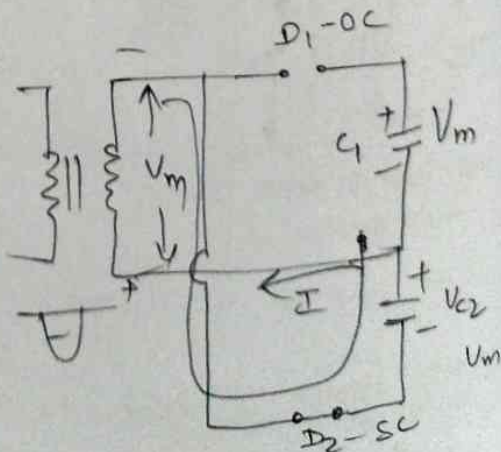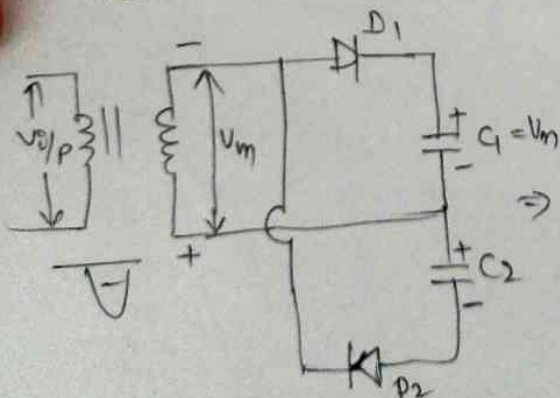

then  $D_1 \rightarrow RB \rightarrow OFF \rightarrow OC$

$D_2 \rightarrow FB \rightarrow ON \rightarrow SC$

→ applying KVL to the above loop

$$\therefore -V_m + V_{C2} = 0$$



$$\therefore V_{C2} = +V_m$$

$\Rightarrow$  during negative half cycle

capacitor  $C_2$  charges to  $+V_m$  volts.

$\therefore$  the output voltage is considered as  $V_{C1} + V_{C2}$

$$\Rightarrow V_{C1} + V_{C2} = V_m + V_m = 2V_m$$

hence the output is double that of the i/p voltage.

hence it's a full wave voltage doubler circuit.

### $\Rightarrow$ Voltage tripler

- A voltage multiplier which produces three times of input voltage at the output then it's called a Voltage-tripler.


- The voltage tripler circuit should have

$\rightarrow$  3 capacitors

$\rightarrow$  3 diodes

In order to produce three times the input voltage as the output voltage

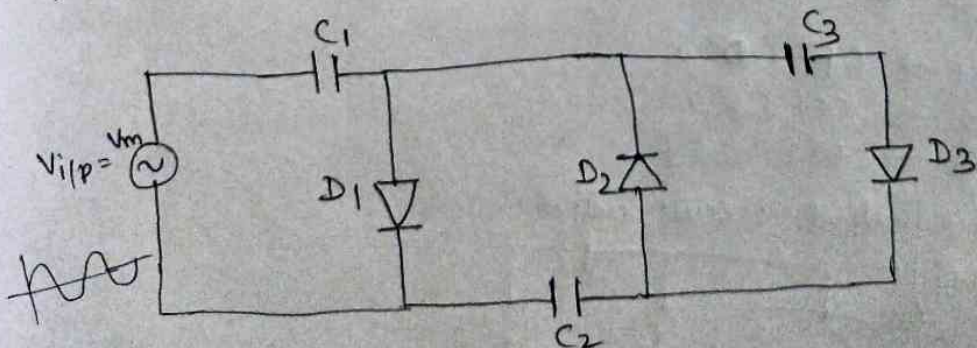
$\Rightarrow$  the circuit diagram is as follows



the output is considered between  $C_1$  and  $C_3$  capacitors

$$\Rightarrow V_{out} = V_{C1} + V_{C3}$$
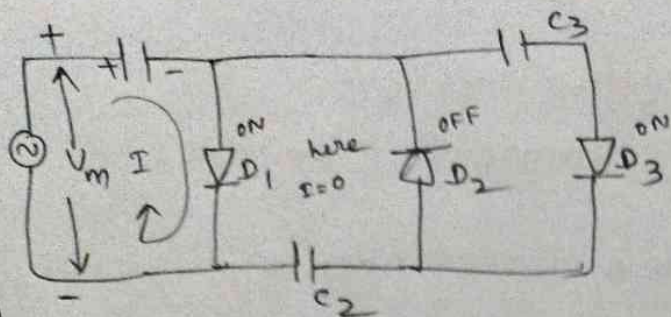
## working of the voltage tripler circuit



(A)


⇒ for positive half cycle of the input

then  $D_1 \rightarrow \text{F.B (ON)} \rightarrow \text{SC}$

$D_2 \rightarrow \text{R.B (OFF)} \rightarrow \text{OC}$

$D_3 \rightarrow \text{F.B (ON)} \rightarrow \text{SC}$

applying the KVL for the above loop.

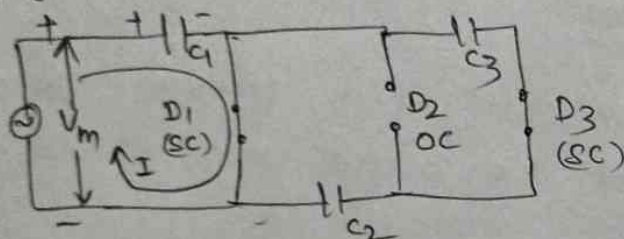

$$\therefore +V_m - V_{C1} = 0$$

$$\therefore \boxed{V_{C1} = +V_m}$$

Capacitor  $C_1 \rightarrow$  charges to  $+V_m$  volts.

during the first +ve half cycle of i/p


⇒ for negative half cycle -

the  $D_1 \rightarrow \text{OFF (OC)}$

$D_2 \rightarrow \text{ON (SC)}$

$D_3 \rightarrow \text{OFF (OC)}$

The equivalent circuit will be

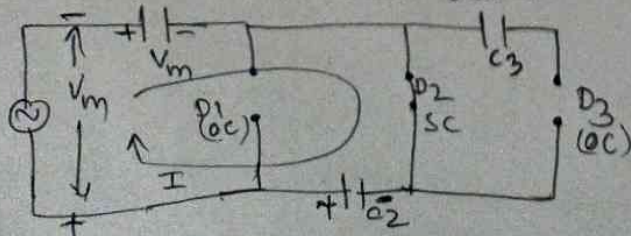



applying KVL for the above loop


$$\Rightarrow -V_m - V_m + V_{C_2} = 0$$

$$\therefore -2V_m + V_{C_2} = 0$$

$$\Rightarrow \boxed{V_{C_2} = +2V_m}$$

$\therefore$  the capacitor  $C_2$  charges to  $2V_m$  volts

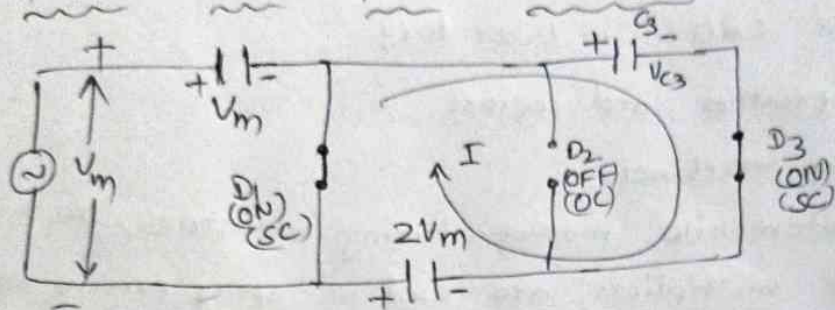$\Rightarrow$  for the next positive half cycle



$D_1$  - ON - SC

$D_2$  - OFF - OC

$D_3$  - ON - SC

Now apply KVL for the following loop  
where we need to determine  $V_{C_3}$

$$\therefore -V_{C_3} + 2V_m = 0$$

$$\therefore \boxed{V_{C_3} = +2V_m}$$

$\Rightarrow$  i.e the capacitor  $C_3$  is charged to  $2V_m$  volts.

As we mentioned the output voltage is considered as voltage between  $C_3$  and  $C_1$  capacitors.

$$\therefore V_{\text{output}} = V_{C_1} + V_{C_3} \\ = +V_m + 2V_m$$

$$\therefore \boxed{V_o = 3V_m}$$

$\therefore$  the output voltage is three times (a) triple of the input voltage.

Hence this circuit is referred as Voltage-tripler.

## Applications of voltage multipliers -

- voltage multipliers are used to produce a DC voltage of few volts to large voltage meant for high energy applications (like physics, electronics experiments).
- some of the applications of voltage multipliers are.
  - used in CRO's in laboratory
  - laser printers and copiers
  - x-ray machines
  - in automobile manufacturing industries, the high voltage multipliers are used in spray painting machines
  - SMPS (switch mode power supplies)
  - etc.